

$$I_{FAULT} = 3I_0 = I_A = 3E / (Z_{S(1)} + Z_{T(1)} + Z_{S(2)} + Z_{T(2)} + Z_{T(0)} + 3Z_E)$$

$$I_{FAULT} \approx 3E / (3Z_E)$$

⑥ $I_{base} = 10,000,000 / (\sqrt{3} \times 13,800) = \underline{418.37 \text{ A}}$


⑦ $I_0 = E / [Z_{S(1)} + Z_{S(2)} + Z_{T(0)}]$
 $I_0 = 1.0 \angle 0^\circ / [j0.052 + j0.052 + j1.33] = 0.697 \text{ pu}$

$I_{FAULT} = 3I_0 = 3 \times 0.697 = 2.091 \text{ pu}$

$I_{FAULT} = I_{FAULT-pu} \times I_{base} = 2.091 \times 418.37 = \underline{874.81 \text{ A}}$

⑧ Current @ the delta winding: $I_\Delta = I_0 \times 418.37 \times 8000/120$

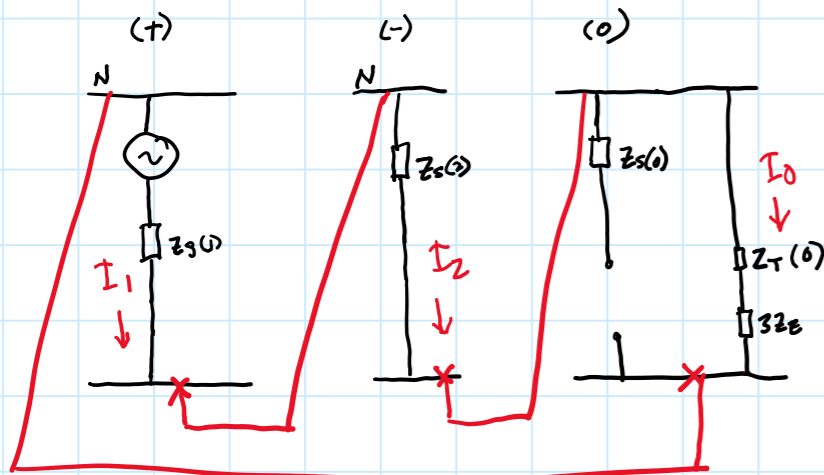$I_\Delta = \underline{19,440.26 \text{ A}}$



Given Data:

① Three-phase fault @ 13.8kV bus is 8kA

② Grounding transformer is a bank of 3 x 50kVA, 8000/120V @ 2%Z

Calculate for Fault Current:

① Choose 10MVA base

② $Z_{base} = 13.8^2 / 10 = \underline{19.044 \Omega}$

③ $Z_{S(1)} = Z_{S(2)} = j [13800 / (\sqrt{3} \times 8000)] = j0.996 \Omega$

④ $Z_{S(1) pu} = Z_{S(2) pu} = j0.996 / 19.044 = \underline{0.052 pu}$

⑤ Given that $Z_E = 20 \Omega$. Calculate for I_{FAULT}

$I_0 = E / [Z_{S(1)} + Z_{S(2)} + Z_{T(0)} + 3Z_E]$


$I_0 = 1.0 \angle 0^\circ / [j0.052 + j0.052 + j1.33 + 3 \times 20 / 19.044]$

$I_0 = 0.2889 \angle -24.47^\circ$

$I_{FAULT} = 3 \times 0.2889 = 0.8667 \text{ pu}$

$I_{FAULT} = 0.8667 \times 418.37 = \underline{362.6 \text{ A}}$

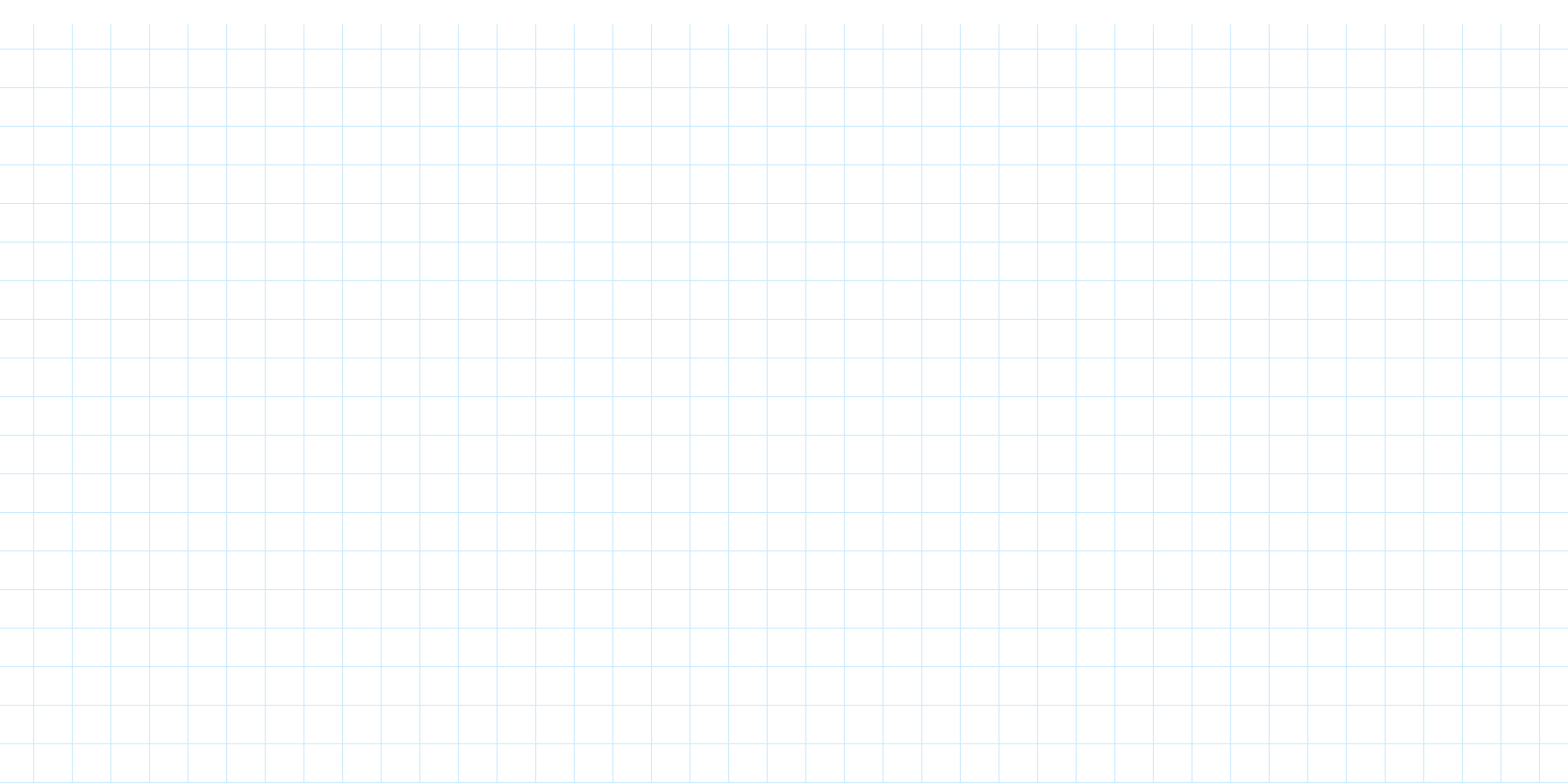$I_\Delta = 0.2889 \times 418.37 \times 8000/120 = \underline{8057.81 \text{ A}}$



$$\textcircled{4} Z_{S(1)} \text{ pu} = Z_{S(2)} \text{ pu} = j0.996 / 19.044 = \underline{0.052 \text{ pu}}$$

$$\textcircled{5} Z_T = j0.02 \times \frac{10,000}{3 \times 50} = 1.33 \text{ pu}$$

