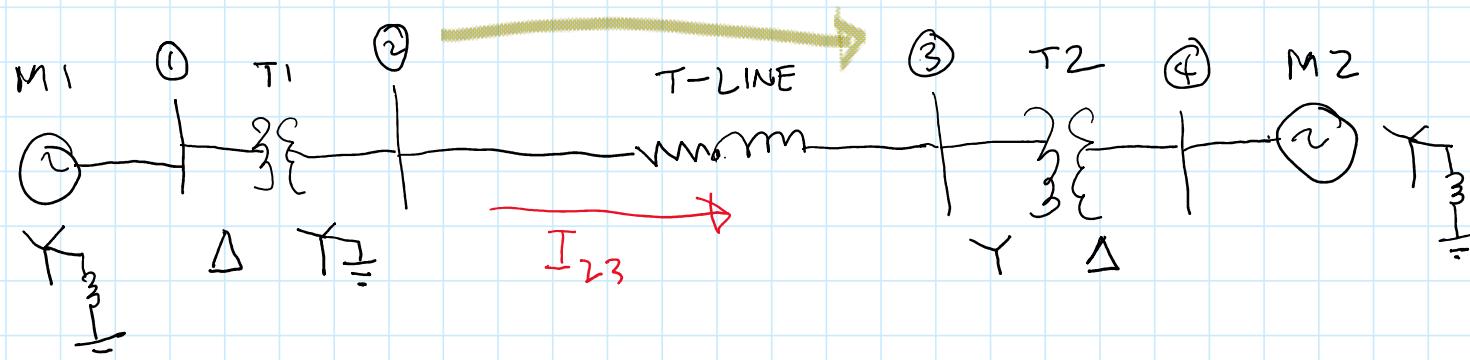


SERIES OR OPEN FAULTS SAMPLE CALCULATIONS



Machines M_1 and M_2 : 100 MVA, 20 kV $X_d'' = X_1 = X_2 = 20\%$; $X_o = 4\%$; $X_n = 5\%$

Transformers T_1 and T_2 : 100 MVA, $20\Delta/345Y$ kV; $x = 8\%$

T-LINE: $X_1 = X_2 = 15\%$; $X_o = 50\%$


REQUIRED: Determine the change in voltage at bus ③ when the transmission line undergoes (a) one-open conductor fault and (b) a two-conductor open fault along its span between buses ② and ③. Consider that Machine #2 is a motor drawing a load equivalent to 60 MVA at 80% power factor lagging and nominal 345 kV voltage at Bus ③.


Steps to calculate for the change in bus voltage due to Open Faults

1. Obtain pre-fault information (load current being delivered)
2. Draw the sequence diagrams (positive, negative, zero-sequence impedance diagrams)
3. Obtain the Bus Impedance Matrix (Zbus matrix) for all three networks
4. Obtain equations for the (+/-/0) sequence impedances as seen from the point of open phase/line conductor
5. Calculate the (+/-/0) sequence voltage drops (equation depends on the type of fault whether one-phase or two-phase open).
6. Calculate the change in the voltage (delta-V) for all three sequences
7. Calculate the final voltage by adding the delta-V and the pre-fault voltage

Modification of existing Z_{bus}

Case	Add branch Z_b from	$Z_{bus \text{ (new)}}$
1	Reference node to new bus (p)	<p>Diagram:</p> <p>Matrix:</p> $(p) \begin{bmatrix} Z_{\text{orig}} & & 0 \\ \hline 0 & \cdots & 0 & & Z_b \end{bmatrix}$
2	Existing bus (k) to new bus (p)	<p>Diagram:</p> <p>Matrix:</p> $\begin{array}{c} \xrightarrow{\quad} (k) \xrightarrow{\quad} (p) \\ \xrightarrow{\quad} (p) \end{array} \begin{bmatrix} Z_{\text{orig}} & & \text{col. } k \\ \hline \text{row } k & & Z_{kk} + Z_b \end{bmatrix}$

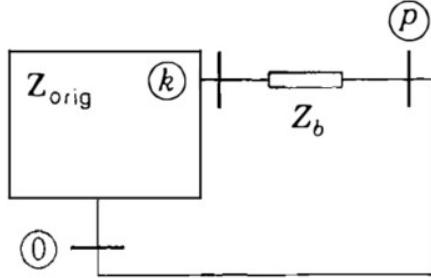	Existing bus (k) to reference node	
3	 <p>(Node (p) is temporary.)</p>	<ul style="list-style-type: none"> • Repeat Case 2 and • Remove row p and column p by Kron reduction

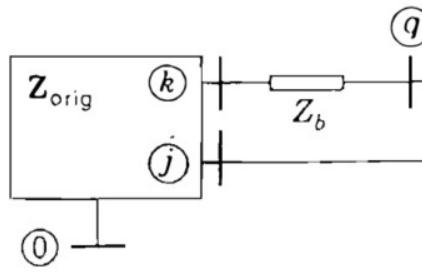
	Existing bus (j) to existing bus (k)	• Form the matrix
4	 <p>(Node (q) is temporary.)</p>	$(q) \left[\begin{array}{c c} Z_{\text{orig}} & \begin{matrix} \text{col. } j - \text{col. } k \\ \hline \end{array} \\ \hline \begin{matrix} \text{row } j - \text{row } k \\ \hline \end{matrix} & Z_{\text{th},jk} + Z_b \end{array} \right]$ <p>where $Z_{\text{th},jk} = Z_{jj} + Z_{kk} - 2Z_{jk}$ and • Remove row q and column q by Kron reduction</p>

STEP #1

Calculate for I_{23} (the current flowing from Bus ② to Bus ③).

Choose 100MVA as Power Base:

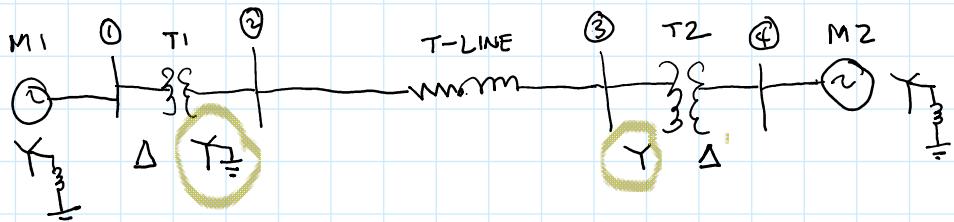
$$I_{23} = \frac{60 / 100 \angle -\cos^{-1} 0.8}{1.0 \angle 0^\circ} = [0.6 \angle -36.87^\circ] \text{ pu}$$



Machines M_1 and M_2 : 100 MVA, 20 kV $X_d = X_1 = X_2 = 20\%$; $X_o = 4\%$; $X_n = 5\%$


Transformers T_1 and T_2 : 100 MVA, $20\Delta/345Y$ kV; $X = 8\%$

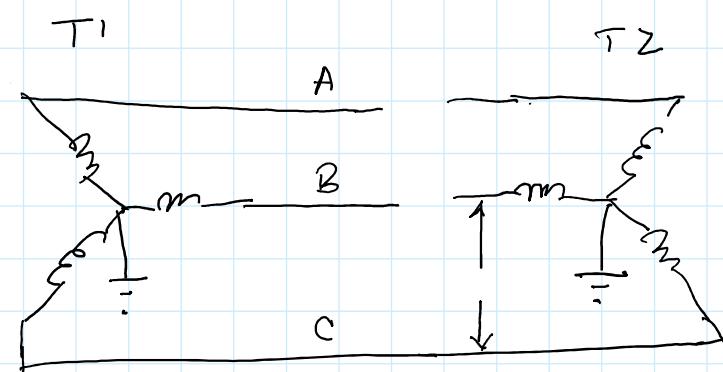T-LINE : $X_1 = X_2 = 15\%$; $X_o = 50\%$




STEP #2 : Draw the Sequence Impedance Networks

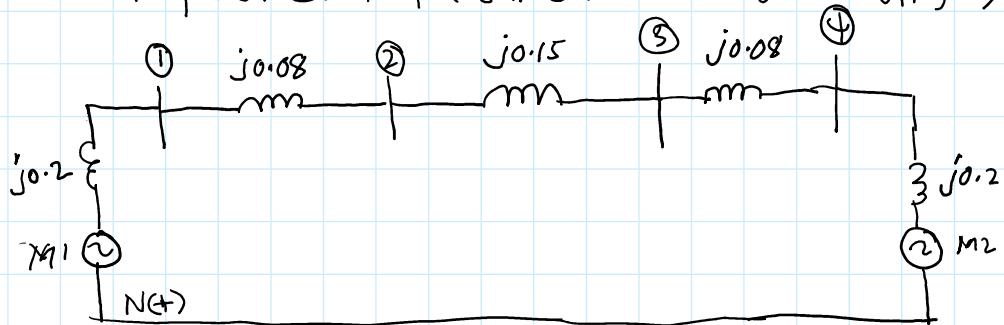
Positive Sequence Impedance (Negative Sequence Impedance is the Same but no Source Voltage)






Zero Sequence Impedance

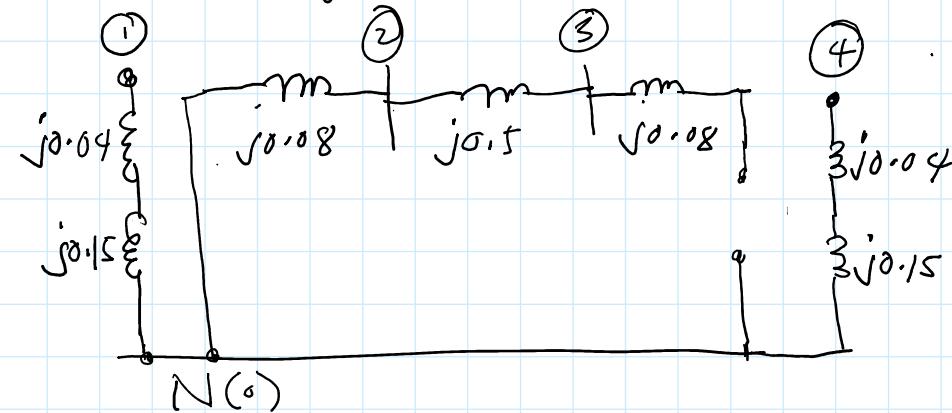

Modification of existing Z_{bus}

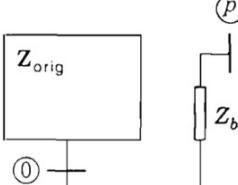Case	Add branch Z_b from	$Z_{bus \text{ (new)}}$
1	Reference node to new bus (\bar{p})	 $(\bar{p}) \left[\begin{array}{c c} Z_{orig} & (\bar{p}) \\ \hline 0 & \begin{matrix} 0 & \vdots \\ \cdots & 0 \end{matrix} \\ & Z_b \end{array} \right]$

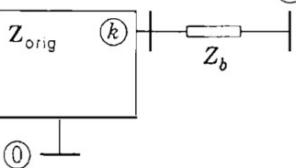
2	Existing bus (k) to new bus (\bar{p})	 $(\bar{p}) \left[\begin{array}{c c} Z_{orig} & col. k \\ \hline row k & Z_{kk} + Z_b \end{array} \right]$
---	---	--

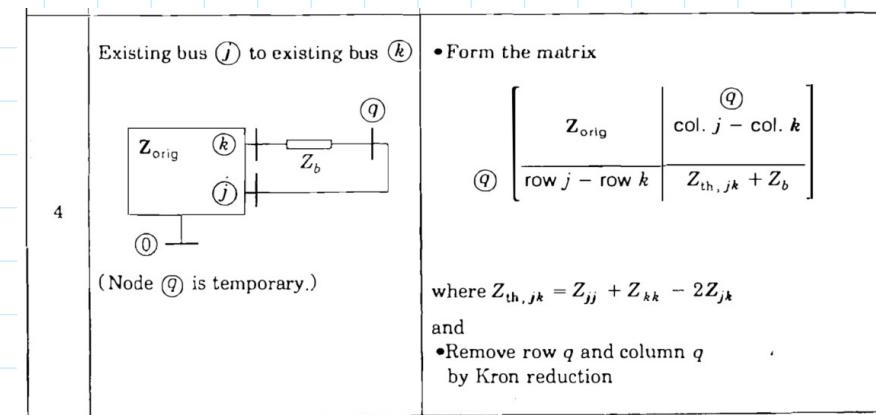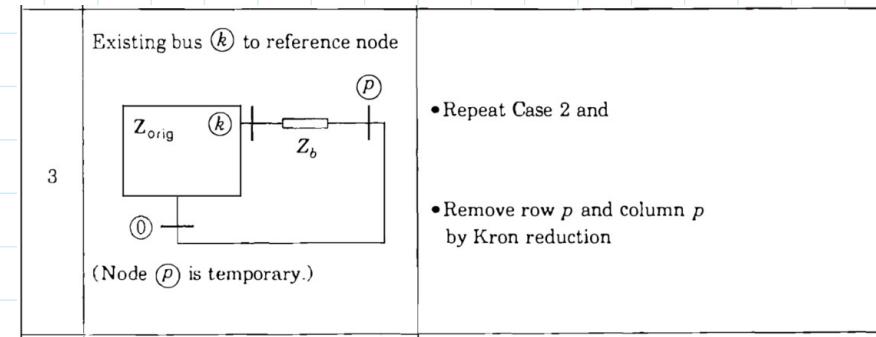




ZBUS
MATRIX

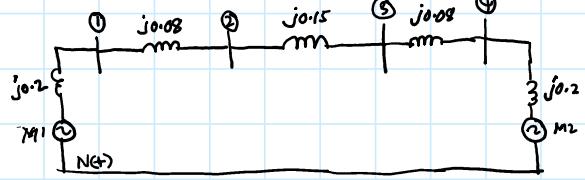Positive Sequence Impedance (Negative Sequence Impedance is the Same but no Source Voltage)



Zero Sequence Impedance

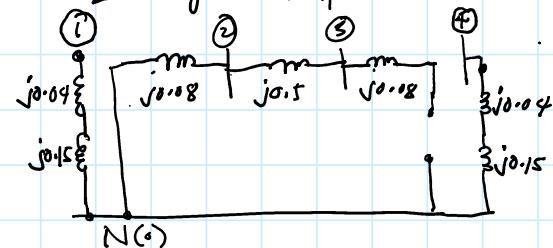


$$\sum_{l=1}^N \sum_{j=1}^N Y'_{ij} = \frac{Y_{ij} - Y_{ik} Y_{jk}}{Y_{kk}}$$





Positive & Negative Seq.

R\c		1	2	3	4
	Bus	1	2	3	4
1	1	0.1437	0.1211	0.0789	0.0563
2	2	0.1211	0.1696	0.1104	0.0789
3	3	0.0789	0.1104	0.1696	0.1211
4	4	0.0563	0.0789	0.1211	0.1437

Zero Sequence



R\c		1	2	3	4
	Bus	1	2	3	4
1	1	0.19	0	0	0
2	2	0	0.08	0.08	0
3	3	0	0.08	0.58	0
4	4	0	0	0	0.19

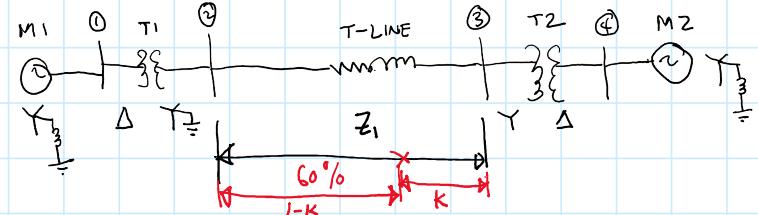

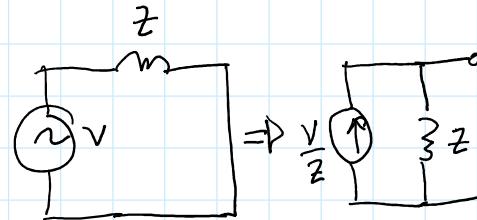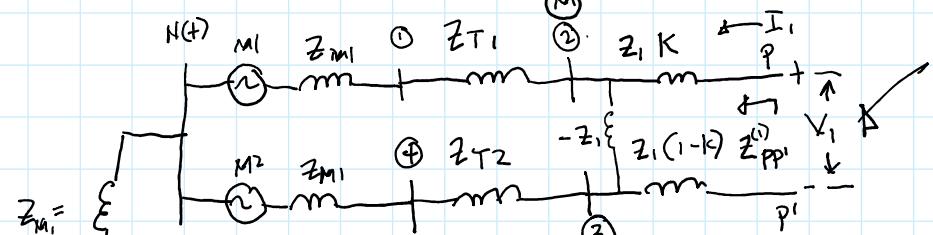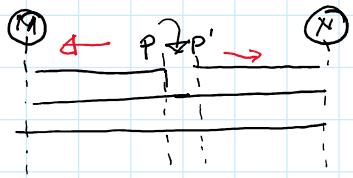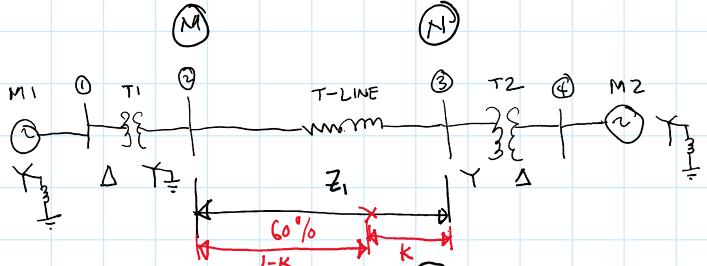

$$Z_{M1} = \frac{V_1}{I_1}$$

$$Z_{M2} = \frac{V_1}{I_2}$$

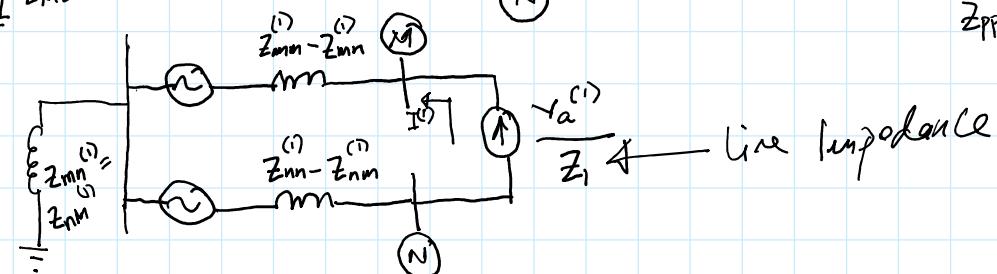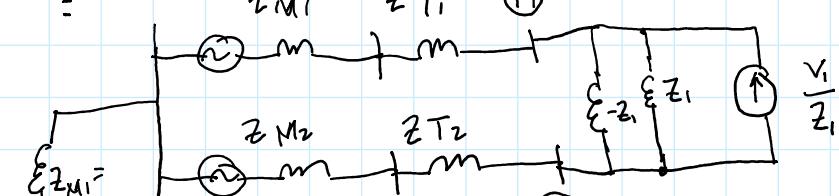

$$Z_{pp'} = k Z_1 + \frac{(-Z_1)(Z_{TH,MN})}{(-Z_1) + (Z_{TH,MN})} + (1-k) Z_1 =$$

$$= \frac{-k Z_1 (Z_{TH,MN}) - k Z_1^2 + (-Z_1)(Z_{TH,MN}) + Z_1 (Z_{TH,MN}) - Z_1^2 - k Z_1 (Z_{TH,MN}) + k Z_1^2}{(Z_{TH,MN}) - (Z_1)}$$

$$Z_{pp'} = \frac{-(Z_1)^2}{(Z_{TH,MN}) - (Z_1)}$$

Impedance as seen from the faulted point
or breaking point of line conductor
(equation applies to positive, negative, zero seq.)

$$\overset{(1)}{Z_{PP}} = \frac{-(Z_1)^2}{(Z_{TH,MN}) - (Z_1)} = \frac{-(j0.15)^2}{(j0.1696) + (j0.1696) - 2(j0.1104) - (j0.15)} = j0.7120 \text{ pu} \quad (\text{positive \& negative seq. impedance})$$

Z_1 = conductor or transmission line Impedance

$Z_{TH,MN}$ = equivalent impedance between bus (1) and bus (M)

Z_{MM} = self impedance of bus (M)

Z_{MN} = transfer impedance between bus (M) and bus (N)

Z_{NN} = self impedance of bus (N)

$Z_{NM} = Z_{MN}$ = transfer impedance between bus (N) and bus (M)


$$Z_{TH,MN} = (Z_{MM} - Z_{MN}) + (Z_{NN} - Z_{NM})$$

$$Z_{TH,MN} = Z_{MM} + Z_{NN} - 2(Z_{MN})$$

$$Z_{MM} = Z_{22} ; Z_{NN} = Z_{33} ; Z_{MN} = Z_{23} ; Z_{NM} = Z_{32}$$

$$\overset{(1)}{Z_{PP}} = \frac{-(Z_1)^2}{(Z_{TH,MN}) - (Z_1)} = \frac{-(j0.5)^2}{(j0.08) + (j0.58) - 2(j0.08) - (j0.5)}$$
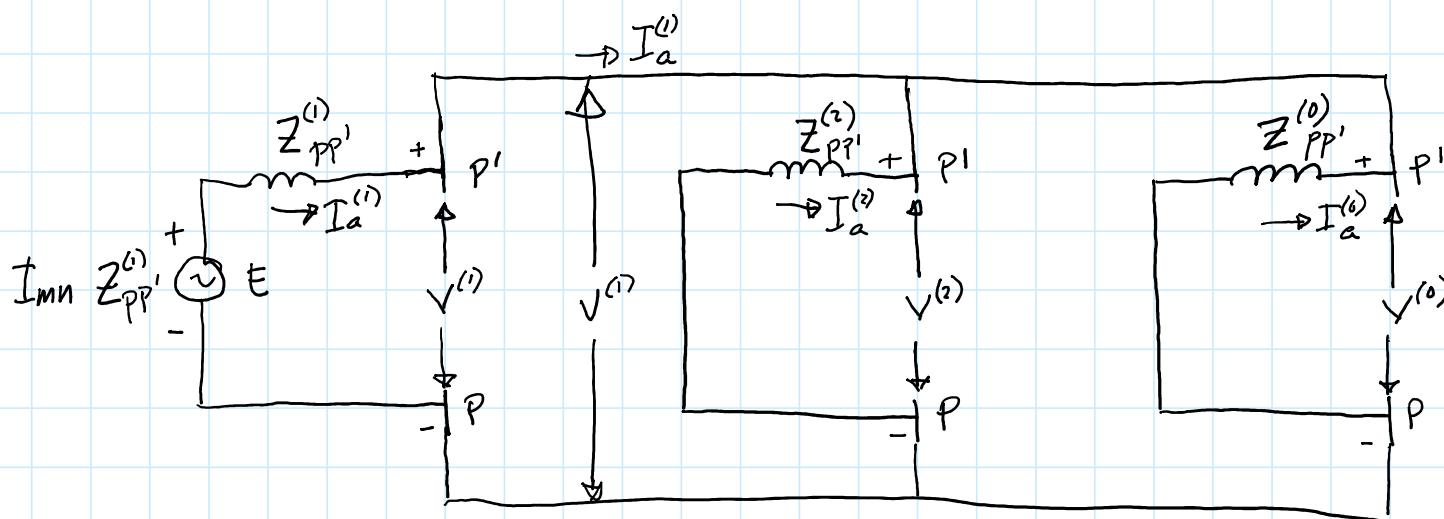
$$\overset{(0)}{Z_{PP}} = \frac{-(j0.5)^2}{0} = \infty \quad (\text{infinite impedance for zero sequence})$$



$$I_a^{(1)} = \frac{E}{Z_{T+}} = \frac{Imn Z_{pp'}^{(1)}}{Z_{pp'}^{(1)} + \frac{Z_{pp'}^{(2)} Z_{pp'}^{(0)}}{Z_{pp'}^{(2)} + Z_{pp'}^{(0)}}} = \frac{Imn Z_{pp'}^{(1)} (Z_{pp'}^{(2)} + Z_{pp'}^{(0)})}{Z_{pp'}^{(1)} Z_{pp'}^{(2)} + Z_{pp'}^{(1)} Z_{pp'}^{(0)} + Z_{pp'}^{(2)} Z_{pp'}^{(0)}}$$

$$V_a^{(1)} = V_a^{(2)} = V_a^{(0)} = \frac{I_a^{(1)} Z_{pp'}^{(2)} Z_{pp'}^{(0)}}{Z_{pp'}^{(1)} + Z_{pp'}^{(0)}} = \frac{Imn Z_{pp'}^{(1)} [Z_{pp'}^{(2)} + Z_{pp'}^{(0)}] [Z_{pp'}^{(2)} Z_{pp'}^{(0)}]}{[Z_{pp'}^{(2)} + Z_{pp'}^{(0)}] [Z_{pp'}^{(1)} Z_{pp'}^{(2)} + Z_{pp'}^{(1)} Z_{pp'}^{(0)} + Z_{pp'}^{(2)} Z_{pp'}^{(0)}]}$$

$$V_a^{(1)} = V_a^{(2)} = V_a^{(0)} = \frac{Imn [Z_{pp'}^{(1)} Z_{pp'}^{(2)} + Z_{pp'}^{(1)} Z_{pp'}^{(0)}]}{Z_{pp'}^{(1)} Z_{pp'}^{(2)} + Z_{pp'}^{(0)} Z_{pp'}^{(1)} + Z_{pp'}^{(1)} Z_{pp'}^{(0)}}$$

$$V_a^{(1)} = V_a^{(2)} = V_a^{(0)} = \frac{Imn [Z_{pp}^{(1)} Z_{pp'}^{(2)} + Z_{pp'}^{(1)} Z_{pp'}^{(0)}]}{Z_{pp'}^{(0)} Z_{pp'}^{(1)} + Z_{pp'}^{(0)} Z_{pp'}^{(2)} + Z_{pp'}^{(2)} Z_{pp'}^{(0)}}$$

$$V_a^{(1)} = V_a^{(2)} = V^{(0)} = \frac{Imn Z_{pp}^{(1)} Z_{pp'}^{(2)}}{Z_{pp'}^{(0)} + Z_{pp'}^{(2)}} = \frac{(0.6 \angle -36.87^\circ)(j0.712)(j0.712)}{j0.712 + j0.712} = 0.2136 \angle 53.13^\circ$$

Current Injections at Bus m

Positive	Negative	Zero
$\frac{\sqrt{(1)}}{Z^{(1)}}$	$\frac{\sqrt{(2)}}{Z^{(2)}}$	$\frac{\sqrt{(0)}}{Z^{(0)}}$

Changes in Voltages

$$\Delta V^{(1)} = \left[-\frac{V^{(1)}}{Z^{(1)}} \right] [Z_{nn} - Z_{nm}] = \left[\frac{V^{(1)}}{Z^{(1)}} \right] [Z_{nm} - Z_{nn}]$$

$$\Delta V^{(2)} = \left[\frac{V^{(2)}}{Z^{(2)}} \right] [Z_m^{(2)} - Z_{nn}^{(2)}]$$

Current Injections at Bus n

positive	Negative	Zero
$-\frac{V^{(1)}}{Z^{(1)}}$	$-\frac{V^{(2)}}{Z^{(2)}}$	$-\frac{V^{(0)}}{Z^{(0)}}$

$$\Delta V^{(0)} = \left[\frac{V^{(0)}}{Z^{(0)}} \right] [Z_{nm}^{(0)} - Z_{nn}^{(0)}]$$

$$\Delta V^{(1)} = \Delta V^{(2)} = \left[\frac{0.2136 \angle 53.13^\circ}{j0.15} \right] [j0.1104 - j0.1696] = 0.0843 \angle -126.87^\circ$$

$$\Delta V^{(0)} = \left[\frac{0.2136 \angle 53.13^\circ}{j0.50} \right] [j0.08 - j0.58] = 0.2136 \angle -126.87^\circ$$

(1)

(2)

(0)

$$\Delta V_3 = \Delta V_3^{(1)} + \Delta V_3^{(2)} + \Delta V_3^{(0)} = (0.0843 \angle -126.87^\circ) + (0.0843 \angle -126.87^\circ) + (0.2136 \angle -126.87^\circ)$$

$$\Delta V_3 = 0.3822 \angle -126.87^\circ$$

Therefore the voltage after the fault:

$$V^{\text{NEW}} = V_3^{\text{PREFAULT}} + \Delta V_3 = (1.0 \angle 0^\circ) + (0.3822 \angle -126.87^\circ) = 0.829 \angle -21.64^\circ \text{ P.U.}$$

$$V^{\text{NEW}} = (0.829)(345 \text{ kV}) = \boxed{286 \text{ kV}}$$