


# Fault Analysis Using Symmetrical Components

## Method to Calculate Unbalanced Short Circuits

- ① Determine simulation points
- ② Find system sequence networks
- ③ Calculate for Thevenin equivalent
- ④ Connect sequence networks and calculate fault currents
- ⑤ Calculate sequence voltages and currents
- ⑥ Calculate phase quantities

# Three-phase fault


## Simplified Generator

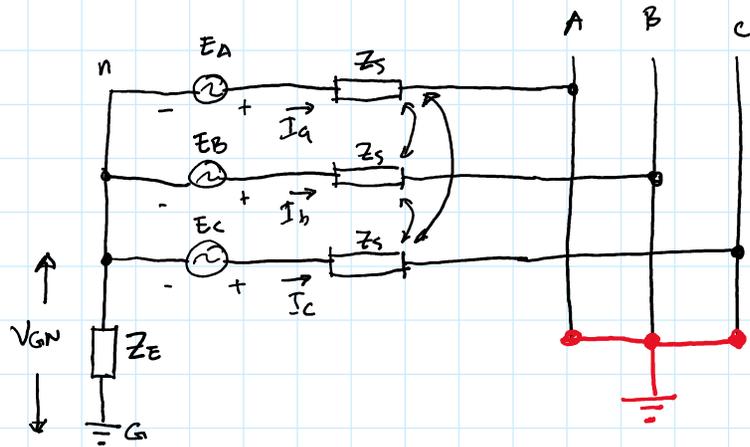

$$I_1 = I_a \checkmark$$

$$I_2 = I_0 = 0$$

$$V_1 = V_2 = V_0 = 0$$

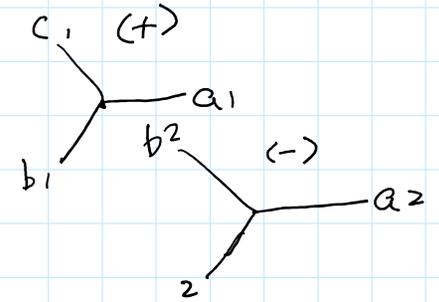

$$I_{B1} = a^2 I_{A1} ; I_{C1} = a I_{A1}$$

Boundary conditions:

$$I_a + I_b + I_c = 0$$

$$V_a = V_b = V_c = 0$$




$$I_2 = 0$$

$$I_0 = 0$$

$$I_1 = \frac{1}{3} (I_A + a I_B + a^2 I_C) = \frac{1}{3} (I_A + a^3 I_A + a^3 I_A) = \frac{1}{3} (3 I_A)$$

$$I_1 = I_A$$
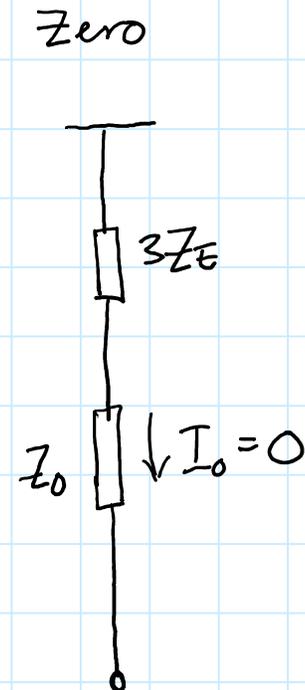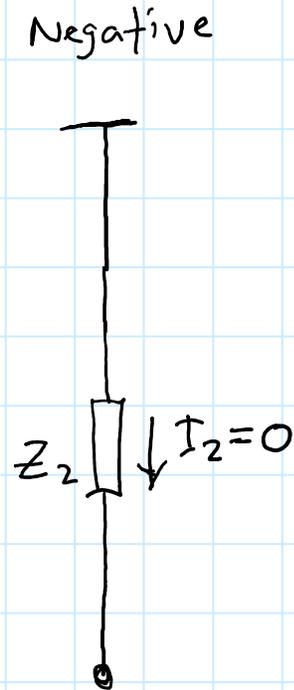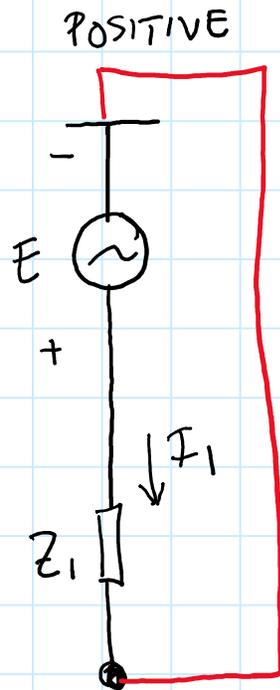
# Three - Phase fault ( Sequence network)




Fault Currents:

$$I_a = I_1 = \frac{E}{Z_1}$$

$$I_b = a^2 I_a$$

$$I_c = a I_a$$

# Phase To Phase Faults

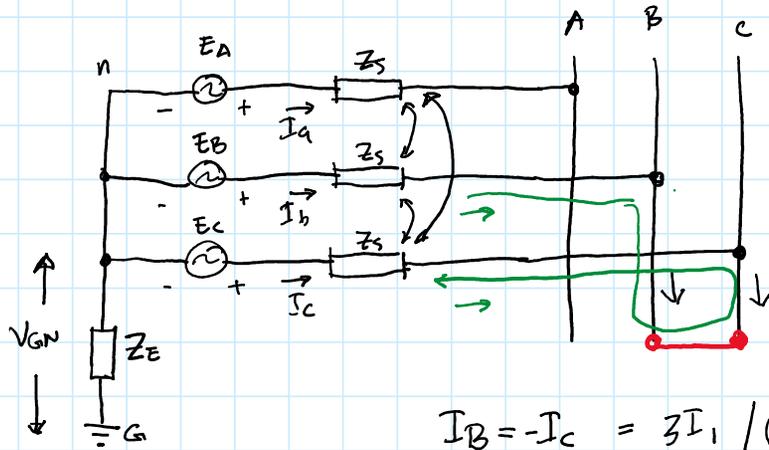

$$I_A = I_{A1} + I_{A2} + I_{A0} = I_1 + I_2 + I_0$$

$$I_B = I_{B1} + I_{B2} + I_{B0} = a^2 I_1 + a I_2 + I_0$$

$$I_C = I_{C1} + I_{C2} + I_{C0} = a I_1 + a^2 I_2 + I_0$$

- ①  $3I_1 = I_A + aI_B + a^2I_C = 0 + aI_B - a^2I_B = I_B(a - a^2)$
- ②  $3I_2 = I_A + a^2I_B + aI_C = 0 + a^2I_B - aI_B = I_B(a^2 - a)$
- ③  $3I_0 = I_A + I_B + I_C = 0 + I_B - I_B = 0$

$$a - a^2 = \sqrt{3} \angle 90^\circ = -j\sqrt{3}$$

$$I_B = -I_C = 3I_1 / (a - a^2) = \frac{-j\sqrt{3} E}{Z_1 + Z_2} = \frac{-j\sqrt{3} E}{2 Z_1}$$

Boundary Conditions:

$$V_b = V_c$$

$$I_A = 0$$

$$I_B = -I_C$$


Note:  $I_{sc} = \frac{E}{Z_1}$

$$I_{LL} = \frac{\sqrt{3}}{2} I_{sc}$$

$$V_1 = V_2$$


$$E = I_1 Z_1 + V_1$$

$$0 = I_2 Z_2 + V_2$$

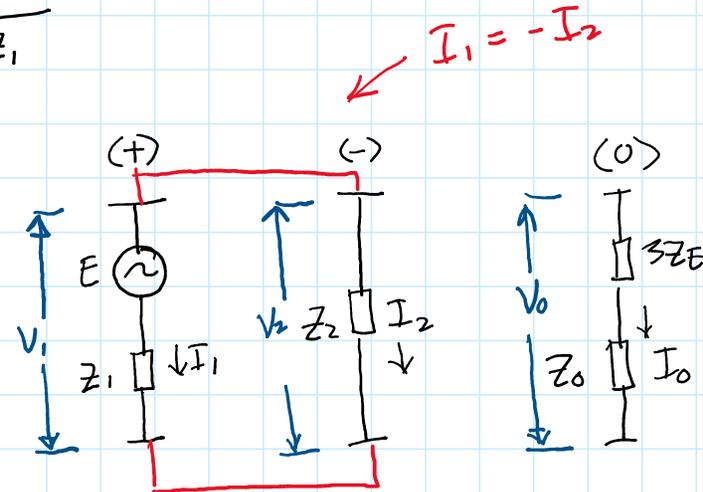


# Symmetrical Components for phase to phase faults

Positive Sequence

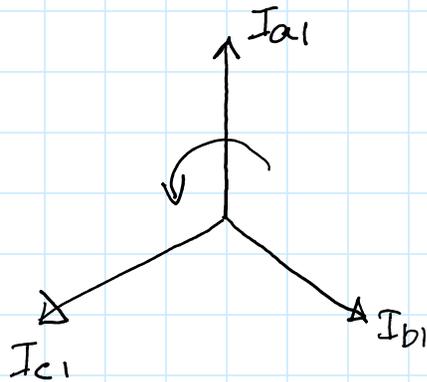




Negative Sequence

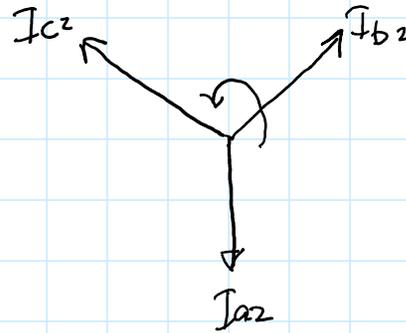


Zero Sequence

Not Participating  
(Equal to zero)

Adding Components

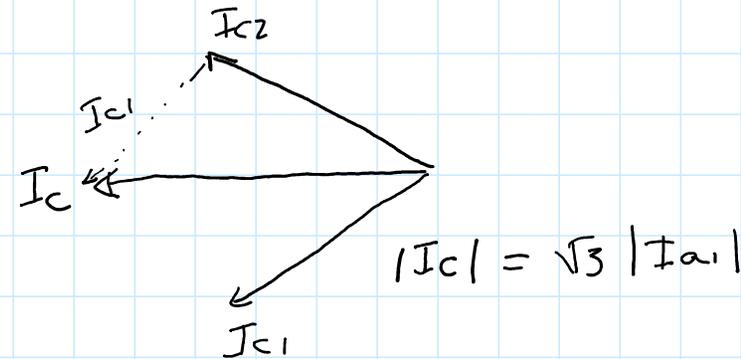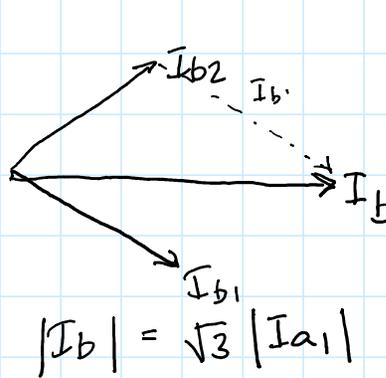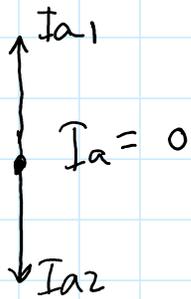

# Single phase TO Ground fault

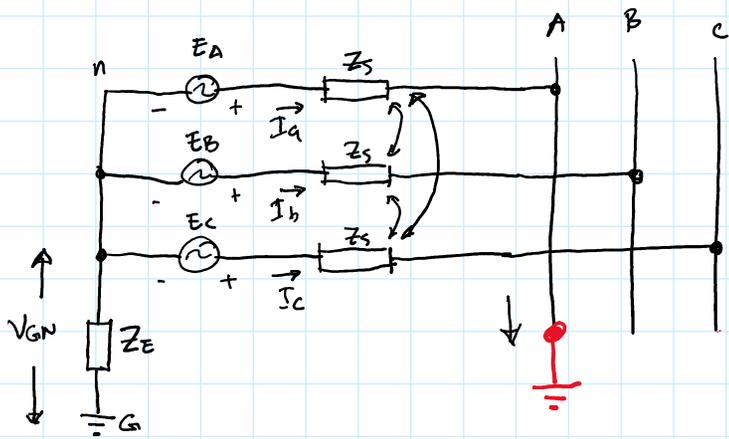

$$I_A = I_{A1} + I_{A2} + I_{A0} = I_1 + I_2 + I_0$$

$$I_B = I_{B1} + I_{B2} + I_{B0} = a^2 I_1 + a I_2 + I_0$$

$$I_C = I_{C1} + I_{C2} + I_{C0} = a I_1 + a^2 I_2 + I_0$$

$$3I_1 = I_A + a I_B + a^2 I_C = I_A$$

$$3I_2 = I_A + a^2 I_B + a I_C = I_A$$

$$3I_0 = I_A + I_B + I_C = I_A$$

$$3I_1 = 3I_2 = 3I_0 = I_A$$

$$I_1 = I_2 = I_0 = \frac{E}{Z_1 + Z_2 + Z_0 + 3Z_E}$$



$$I_A = 3I_0 = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_E}$$

Boundary Conditions:

$$V_a = 0 ; I_b = I_c = 0$$

3-Leg Core Type :  $Z_0 \approx 0.8 - 0.9 Z_1$

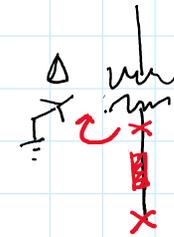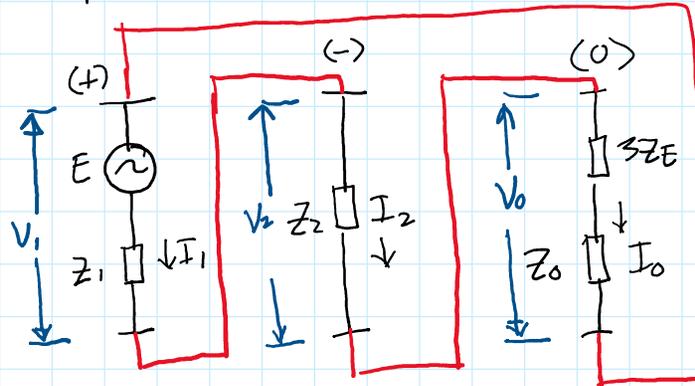Shell Type }  
 Four leg core type }  $Z_0 = Z_1 = Z_2$   
 Five leg core type }  
 Banks of  $3 \times I\phi$  }



Fault near X<sub>FN</sub> or Neutral




$$I_A = 3I_0 = \frac{3E}{Z_1 + Z_2 + Z_0}$$

For core type (3-leg)

$$SLG-I_A = \frac{3E}{2.8 Z_1} ; I_{3\phi} = \frac{E}{Z_1}$$

Therefore  $I_{1\phi} = 107\% I_{3\phi}$

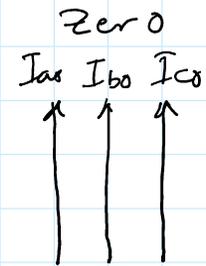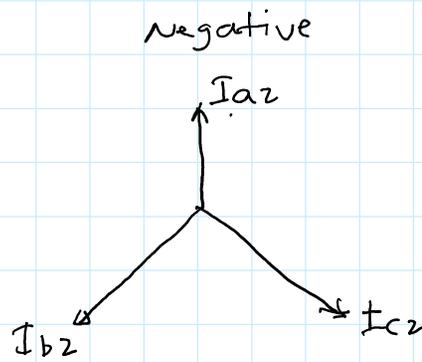
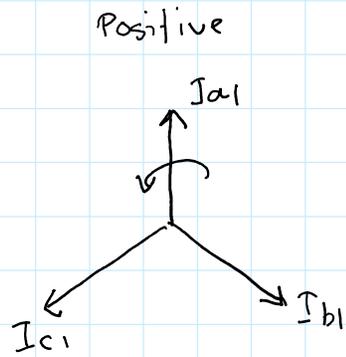
# Symmetrical Components for A-phase-to-Ground Fault




$$I_A = I_{a1} + I_{a2} + I_{a0}$$

$$I_B = I_{b1} + I_{b2} + I_{b0} = 0$$

$$I_C = I_{c1} + I_{c2} + I_{c0} = 0$$

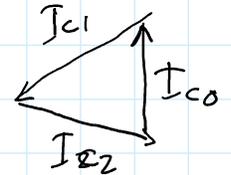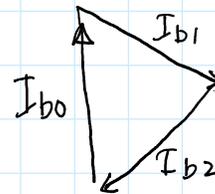

Phase To Phase To Ground

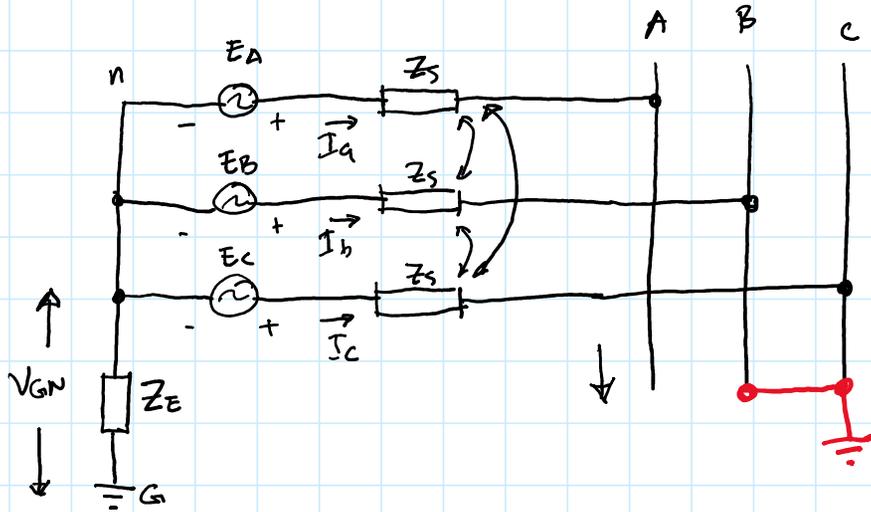

$$I_{A0} = \frac{1}{3}(I_A + I_B + I_C) = \frac{1}{3}(I_B + I_C)$$

$$V_B = V_C = 3I_{A0} Z_E$$

$$V_0 = \frac{1}{3}(V_A + V_B + V_C) \rightarrow \textcircled{2}$$

$$V_1 = \frac{1}{3}(V_A + aV_B + a^2V_C)$$

$$V_2 = \frac{1}{3}(V_A + a^2V_B + aV_C) \quad \left. \vphantom{V_1, V_2} \right\} \textcircled{1}$$


Since  $V_B = V_C$

$$\textcircled{1} \quad V_1 = V_2 = \frac{1}{3}(V_A + aV_B + a^2V_B) = \frac{1}{3}(V_A + aV_C + a^2V_C)$$

$$\textcircled{2} \quad 3V_0 = V_A + 2V_B = (V_0 + V_1 + V_2) + 2(3I_0 Z_E)$$

Boundary Conditions:
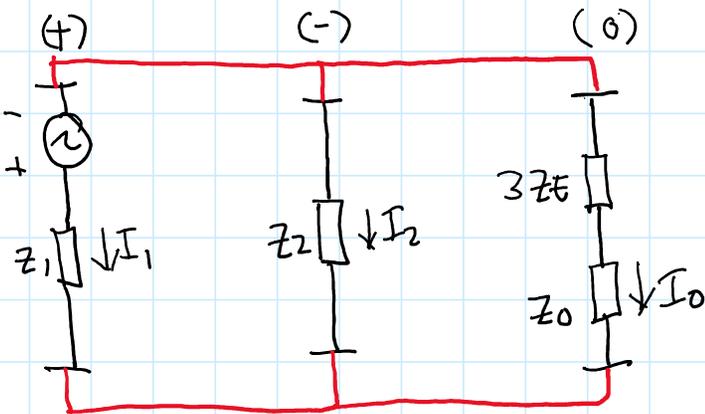
$$I_A = 0 \quad V_B = V_C = (I_A + I_B) Z_E$$



$$3V_0 = (V_0 + 2V_1) + 2(3I_0 Z_E)$$




$$2V_1 = 2V_0 - 2(3I_0 Z_E)$$

$$V_1 = V_0 - 3I_0 Z_E$$



$$V_1 = V_2 = V_0 - 3I_0 Z_E$$

$$I_1 + I_2 + I_0 = 0 \quad (\text{Taking Phase A as reference})$$
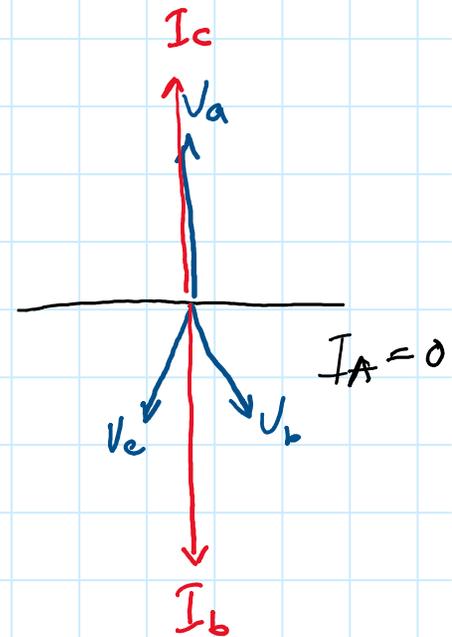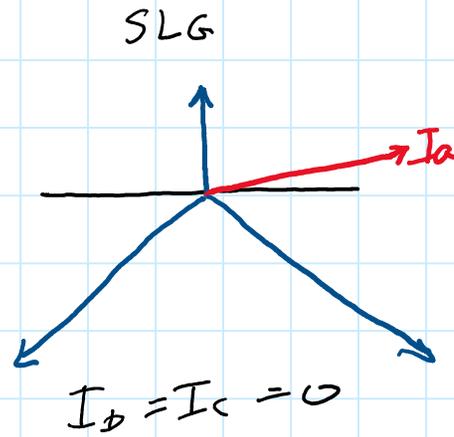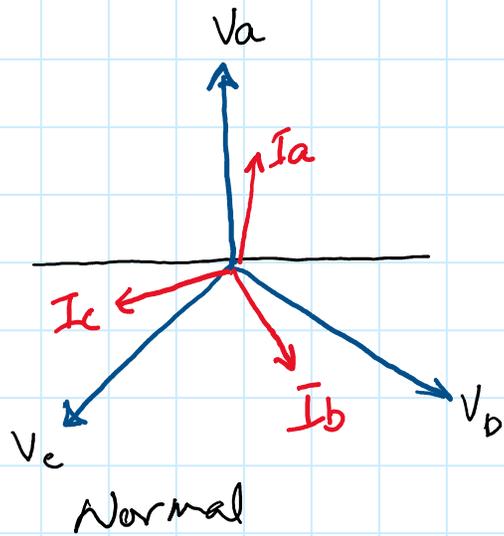
# Phasor Voltage and Current Behaviour During Fault


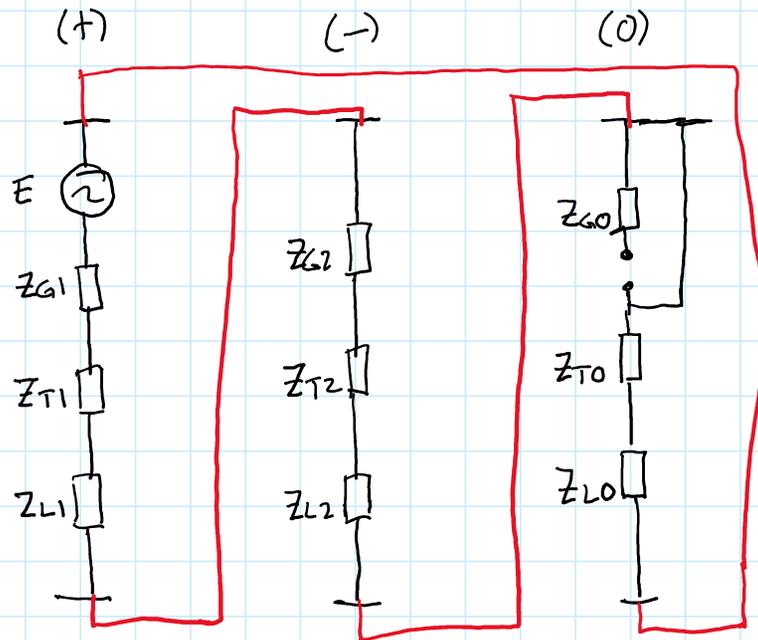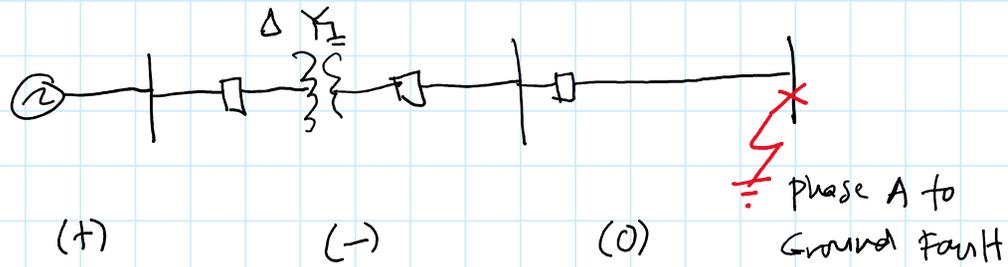
# Single-Phase Phase to Ground Fault (Radial System)



$$Z_{TOTAL} = Z_{G1} + Z_{T1} + Z_{L1} + Z_{G2} + Z_{L2} + Z_{T0} + Z_{L0}$$

$$I_{FAULT} = \frac{E}{Z_{TOTAL}}$$

# Sequence Networks of Two-Source Power System

3 $\phi$  Fault:  $Z_{TOTAL} = \left( \frac{1}{Z_{S1} + Z_{L1}} + \frac{1}{Z_{R1}} \right)^{-1}$

