



Series Faults:

Causes: Broken Conductors, Blown Fuses, Open-Pole Condition

Effects: System Unbalance (negative and zero sequence)

Consideration: System load (Load Current)

# One-phase Open

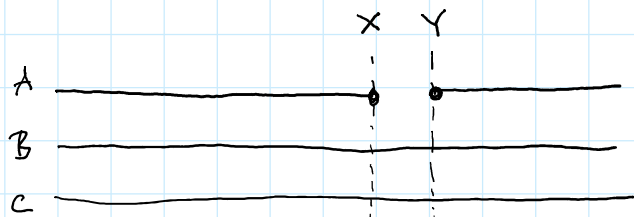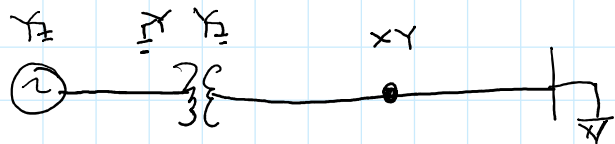

Boundary Conditions:

$$I_A = 0 ; \quad \underline{V_{BXY}} = 0 ; \quad \underline{V_{CXY}} = 0$$


Solving for Sequence Quantities (Using Phase A as Reference)  
 Since  $I_A = 0$ , then  $I_A = I_1 + I_2 + I_0 = 0$

$$3V_{0XY} = V_A + V_B + V_C = V_A$$



$$3V_{1XY} = V_A + aV_B + a^2V_C = V_A$$

$$3V_{2XY} = V_A + a^2V_B + aV_C = V_A$$


$$V_1 = V_2 = V_0 = V_A$$

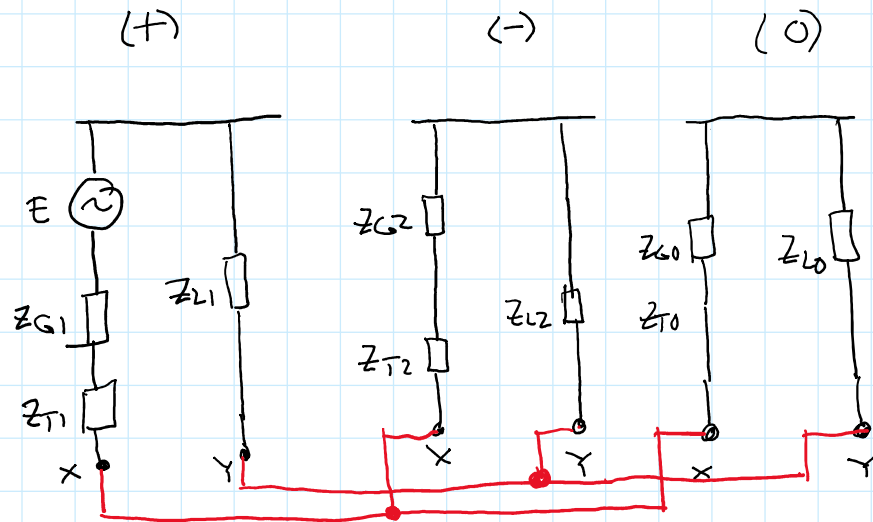



# One Phase Open Delta-Wye Transformer:

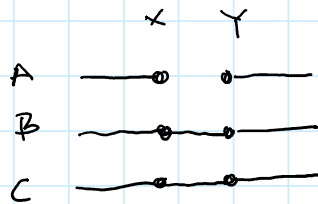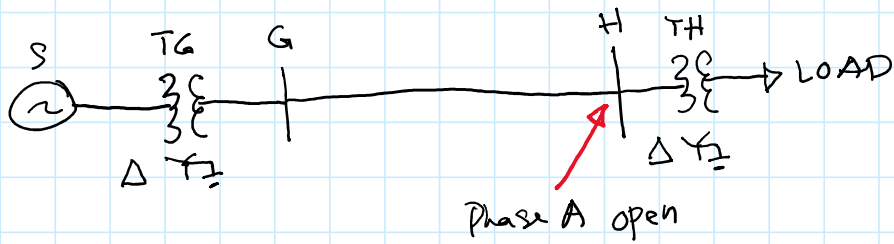


NOT Participating  
Due to Delta

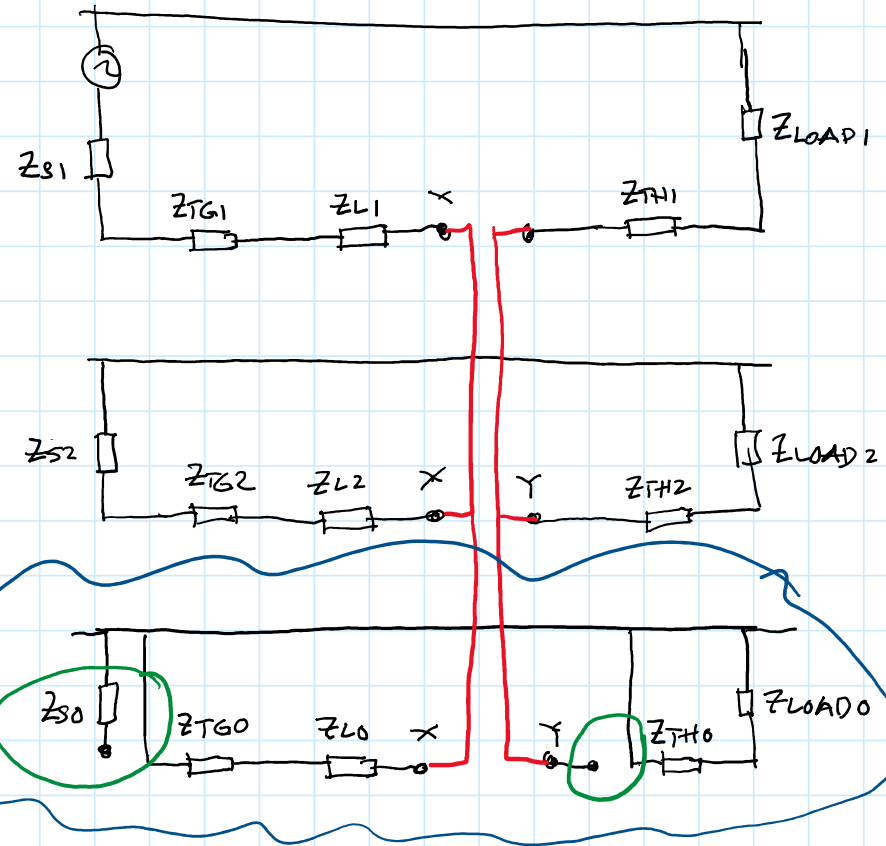


# One Phase Open Wye-Delta Transformer:

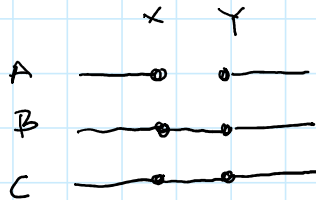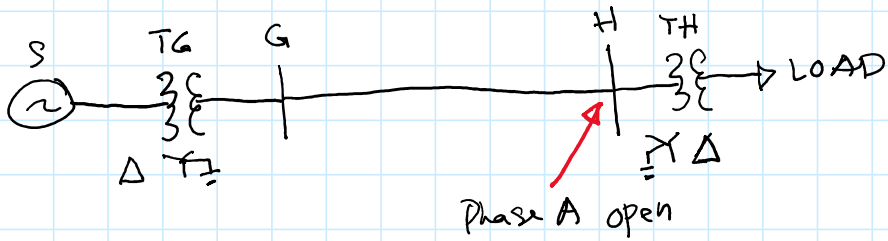

Participating  
Due to Wye-Delta  
XFMR

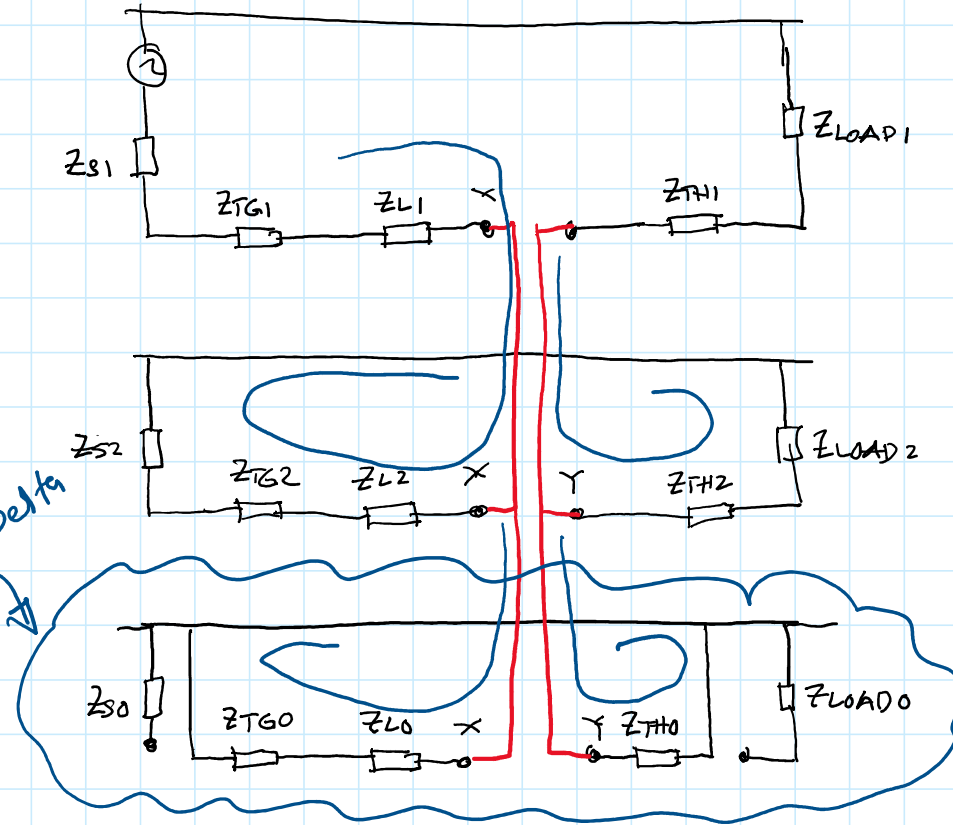


# Series Fault Two-Phase Open

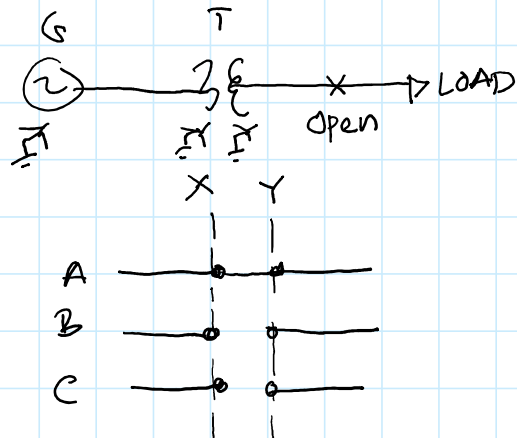


Boundary Conditions:  
 $I_B = I_C = 0$   
 $V_{XY} = 0$

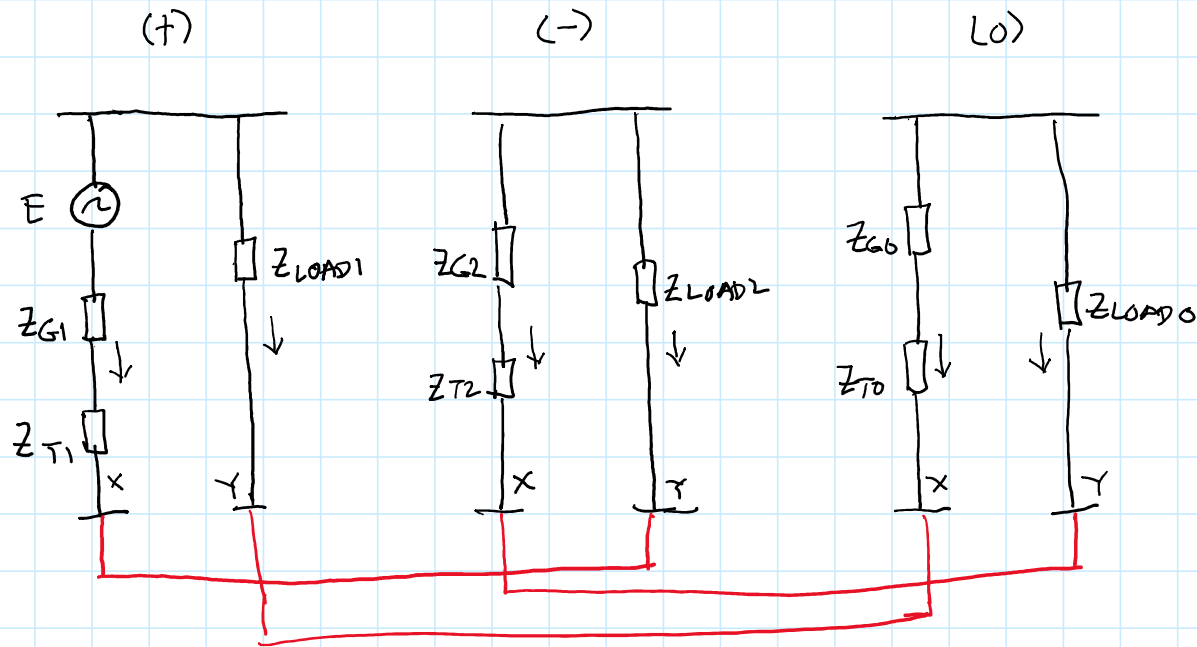
$$\begin{aligned} 3I_0 &= I_A + \cancel{I_B} + \cancel{I_C} &= I_A \\ 3I_1 &= I_A + \cancel{a^2 I_B} + \cancel{a I_C} &= I_A \\ 3I_2 &= I_A + \cancel{a^2 I_B} + \cancel{a I_C} &= I_A \\ I_0 &= I_1 = I_2 = \frac{1}{3} I_A \end{aligned}$$





# Two Phase Open Delta-Wye Transformer:

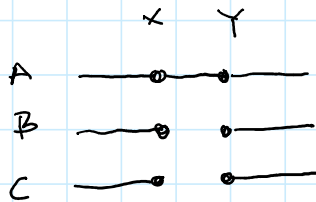


$$I_{IG} = I_{IG} = I_{IG} = 0$$

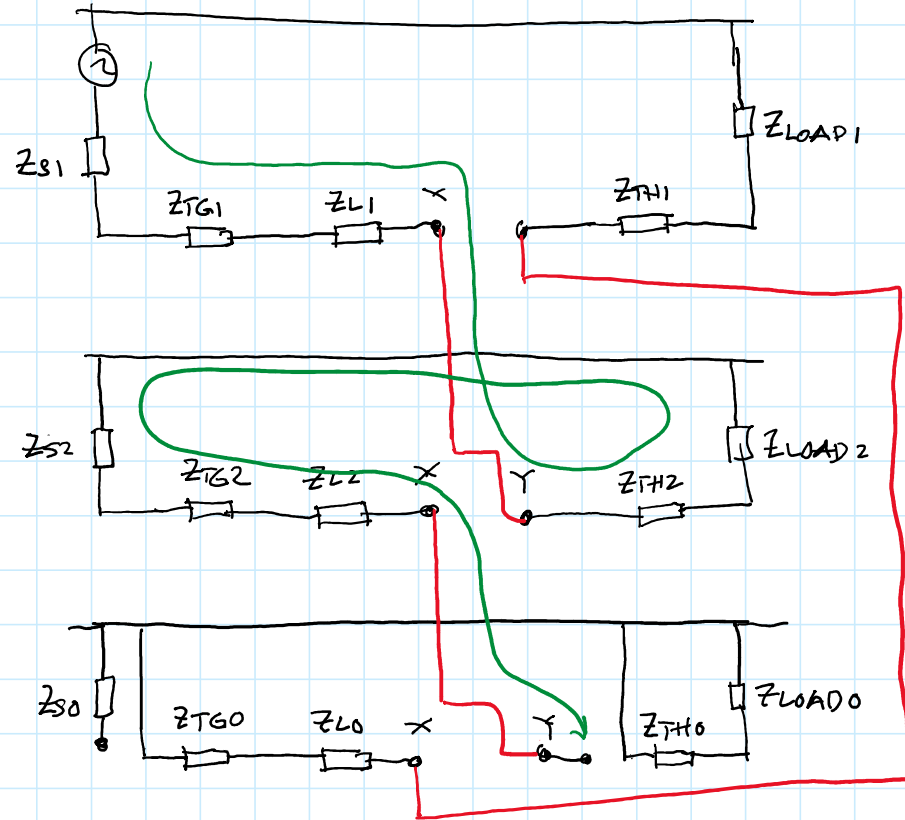

# Two Phase Open Wye-Delta Transformer:

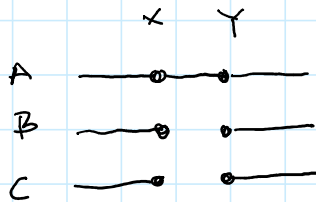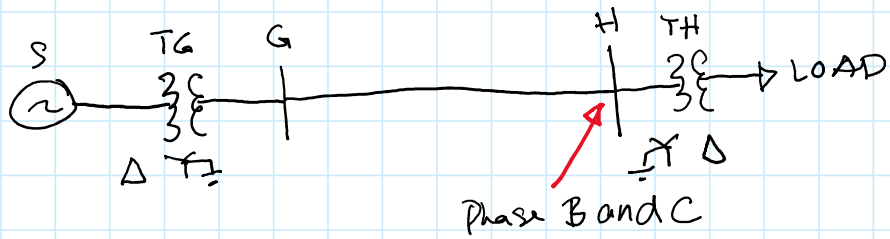
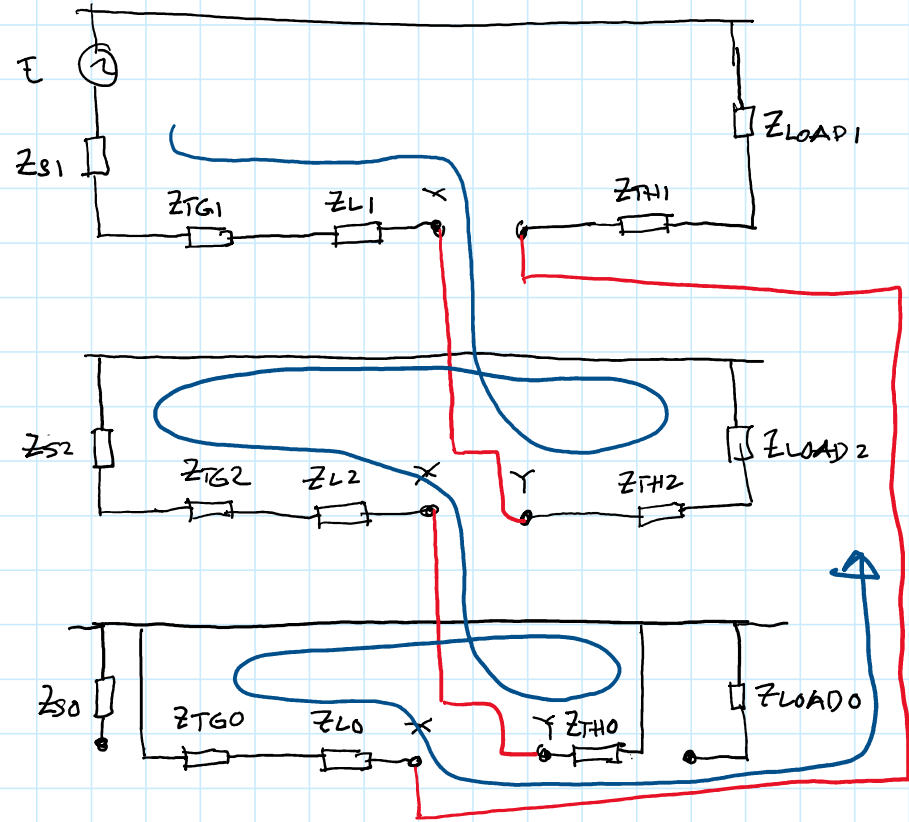
$$I_G = I_{2G} = I_{0G} \quad I_G = \frac{E}{Z_1 + Z_2 + Z_0}$$



# Symmetrical Components Present During Faults

	Both Sides Grounded	one side Grounded
One phase open	1, 2, 0	1, 2
Two phases open	1, 2, 0	None