


$$I_{\text{FAULT}} = 3E / (Z_{S1} + Z_{S2} + Z_{T1} + Z_{T2} + Z_{T0} + 3Z_E)$$

$$Z_E \gg Z_S$$


$$Z_E \gg Z_T$$

Therefore: $I_{\text{FAULT}} \approx E / Z_E$


Using Grounding Transformer

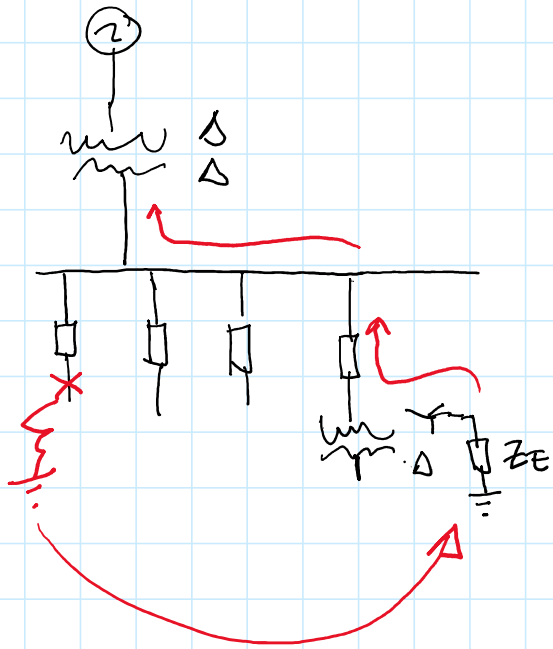

$3\phi, L_L, SUG$
 LLG

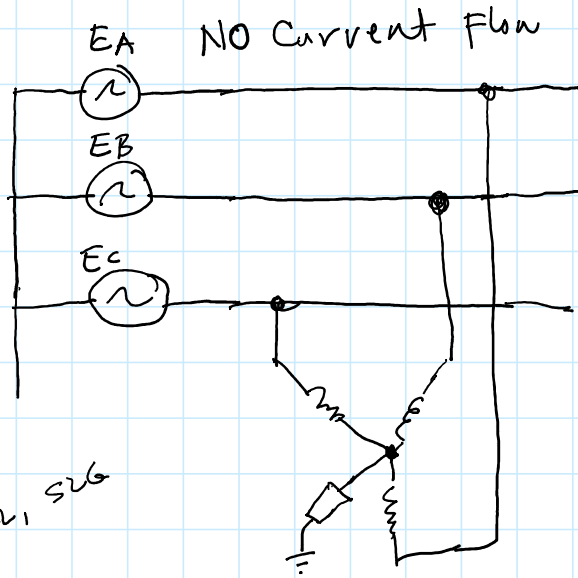

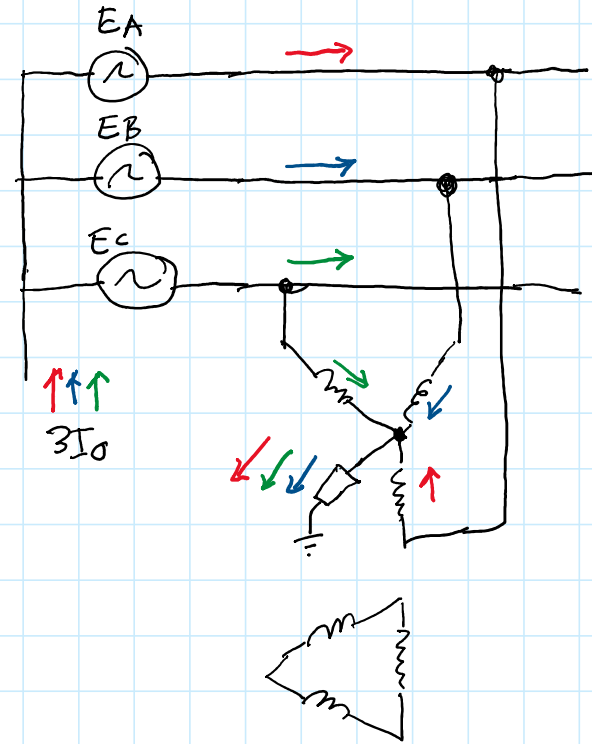Response for positive
and Negative Sequence
Currents



Response for Zero Sequence