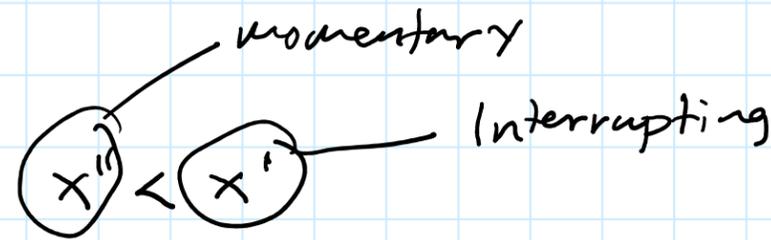


✓ Momentary = 1/2 cycle → Utility, local generators, motors → Bus bracing, Fast acting fuses, ✓



✓ Interrupting = 1.5 - 4 cycle → Utility, local generators → Breakers, Relays (Instantaneous)


✓ Steady state = 30 cycle → Utility → Breaker, Relays (time-delayed)

X'' - subtransient reactance
 X' - transient reactance



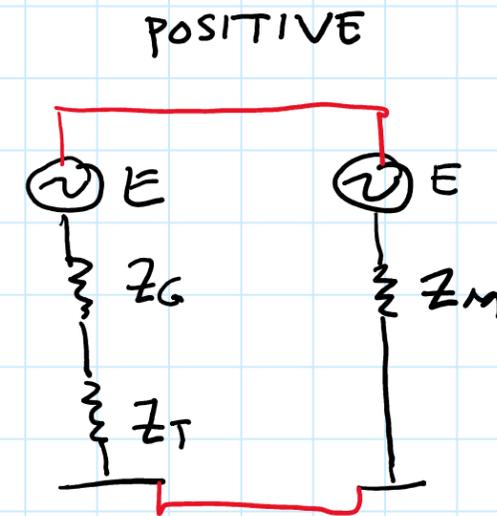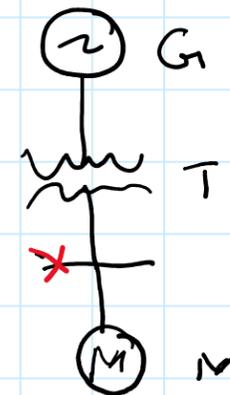$X'' = 20\% = 0.2 \text{ pu} \rightarrow 1/2 \text{ cycle}$
 $X' = 50\% = 0.5 \text{ pu} \rightarrow 1.5 - 4 \text{ cycle}$



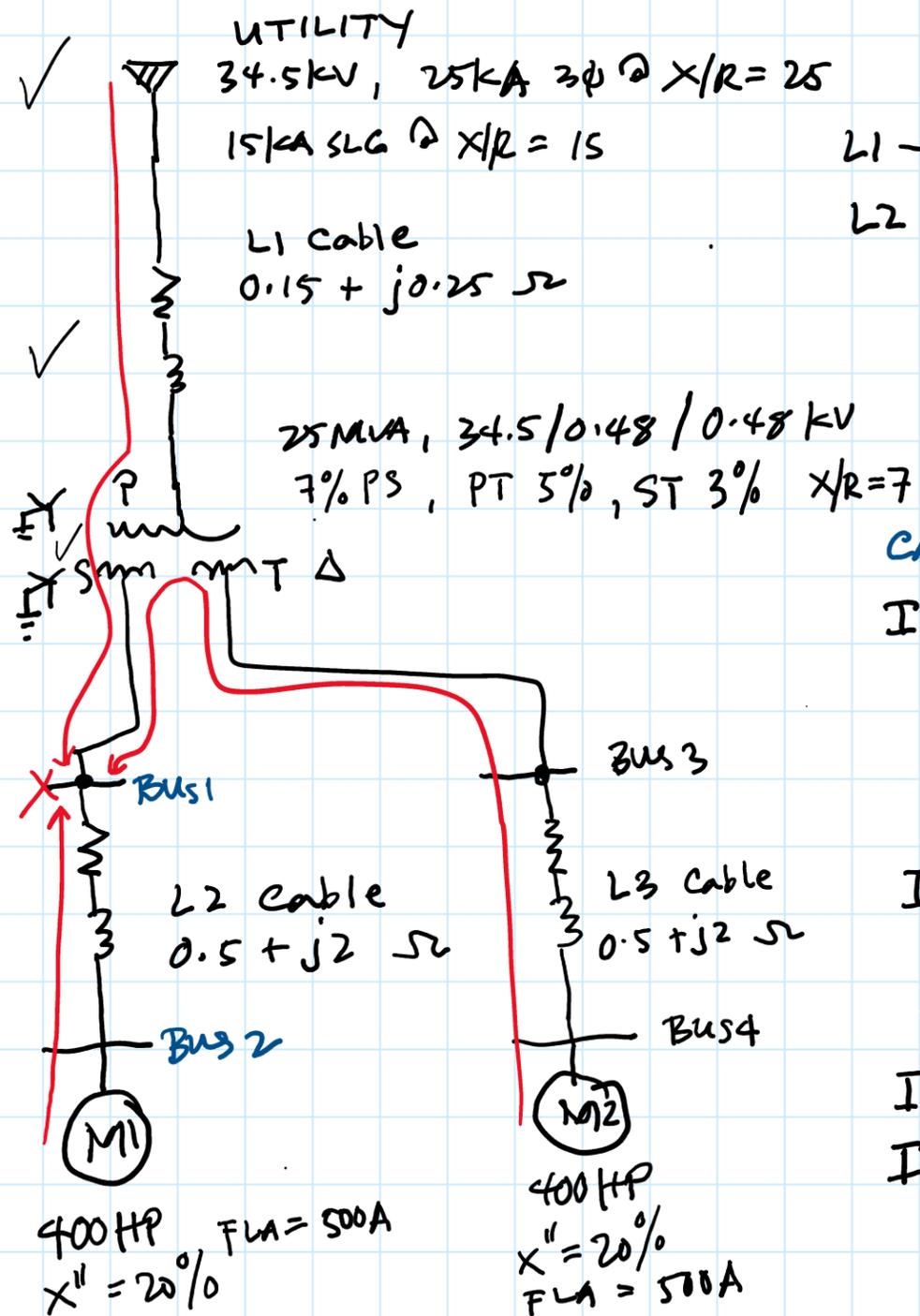

CABLE IMPEDANCES

$$L1 \rightarrow Z_1 = Z_2 = Z_0 = (0.15 + j0.25) / 119.025 = 0.002449 \angle 59.04^\circ \text{ pu}$$

$$L2 \rightarrow Z_1 = Z_2 = Z_0 = (0.5 + j2) / 0.02304 = 89.4771 \angle 75.96^\circ \text{ pu}$$

TRANSFORMER IMPEDANCE

$$Z_1 = Z_2 = Z_0 = 0.07 (10/25) = 0.028 \angle 81.87^\circ$$

CALCULATE FOR A 3 ϕ FAULT CURRENT @ BUS2

$$I_{3\phi} = E / Z_{TH} = 1.0 \angle 0^\circ / (Z_{1U} + Z_{1L1} + Z_{1T} + Z_{1L2})$$

$$= 1.0 \angle 0^\circ / (0.006694 \angle 87.7^\circ + 0.002449 \angle 59.04^\circ + 0.028 \angle 81.87^\circ + 89.4771 \angle 75.96^\circ)$$


$$= 0.01117 \angle -75.96^\circ \text{ pu}$$

$$I_{3\phi} = 0.01117 \angle -75.96^\circ \times 12028.13 = \boxed{134.35 \angle -75.96^\circ \text{ A}}$$

3 ϕ FAULT @ BUS1

$$I_{3\phi} = E / Z_{TH} = 1.0 \angle 0^\circ / (Z_{1U} + Z_{1L1} + Z_{1T}) = 27.0875 \angle -81.45^\circ \text{ pu}$$
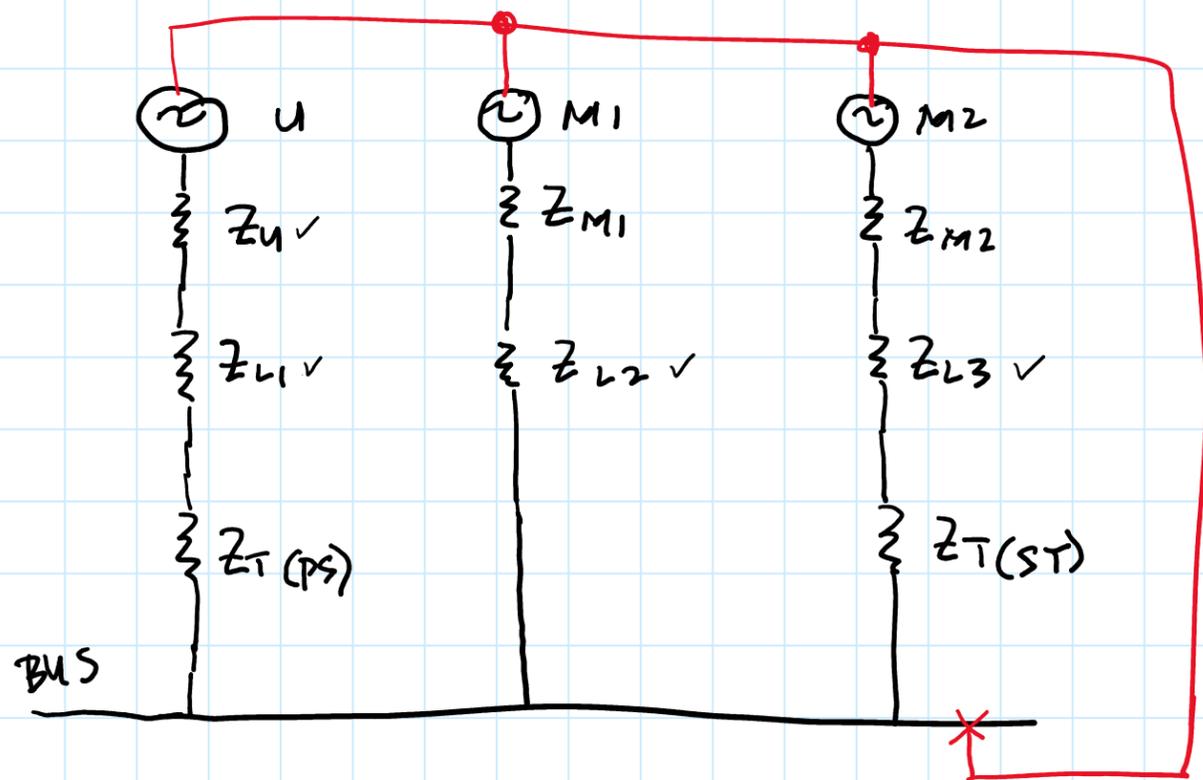
$$I_{3\phi} = 27.0875 \angle -81.45^\circ \times 12028.13 = \boxed{325,811.97 \angle -81.45^\circ \text{ A}}$$



$$Z_{1U} = 0.006694 \angle 87.71^\circ \rightarrow A$$

$$Z_{1L1} = 0.002449 \angle 59.04^\circ \rightarrow B$$

$$Z_{1L2} = Z_{1L3} = 89.4771 \angle 75.96^\circ \rightarrow C$$

$$Z_{T(PS)} = 0.028 \angle 81.87^\circ \rightarrow D$$

$$Z_{T(ST)} = 0.03 (10/25) = 0.012 \angle 81.87^\circ \rightarrow E$$

$$Z_{M1} = Z_{M2} = 0.2 (10/0.4) = j5 \text{ pu} \rightarrow F$$

$$Z_{TH} = \left[\begin{array}{c} A \quad B \quad D \quad F \quad C \\ (Z_U + Z_{1L1} + Z_{T(PS)})^{-1} + (Z_{M1} + Z_{1L2})^{-1} + \\ (Z_{M2} + Z_{1L3} + Z_{T(ST)})^{-1} \end{array} \right]^{-1}$$

$$Z_{TH} = 0.036889 \angle 81.45^\circ$$


$$I_{pu} = 1 \angle 0^\circ / Z_{TH} = 27.1086 \angle -81.45^\circ$$

$$I_F = I_{pu} \times I_b = 27.1086 \times 12028.13 \\ = 326,065.77 \text{ A}$$


PHASOR VOLTAGE & CURRENT BEHAVIOR DURING FAULTS

THREE PHASE FAULTS


NORMAL OPERATION

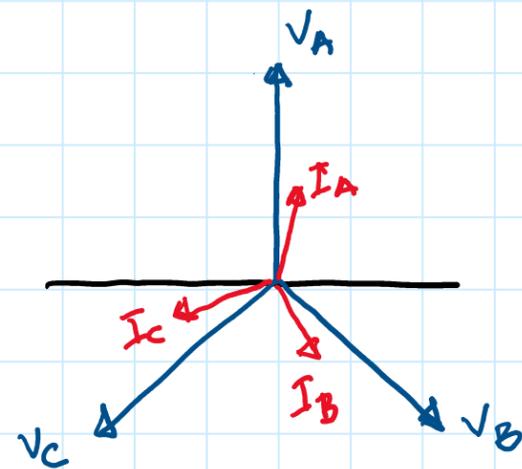


3-PHASE FAULT

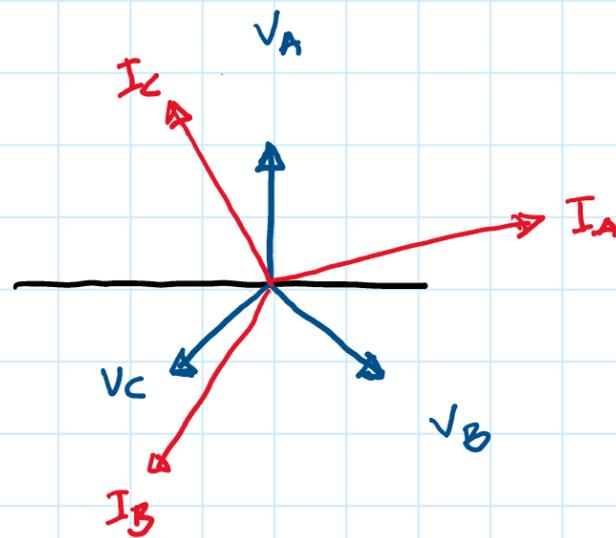


SLG

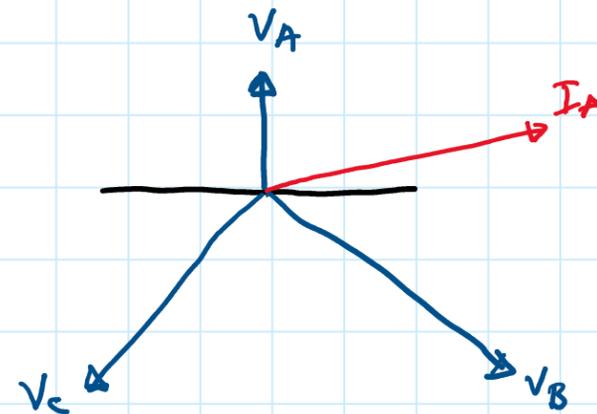

DOUBLE LINE TO GROUND





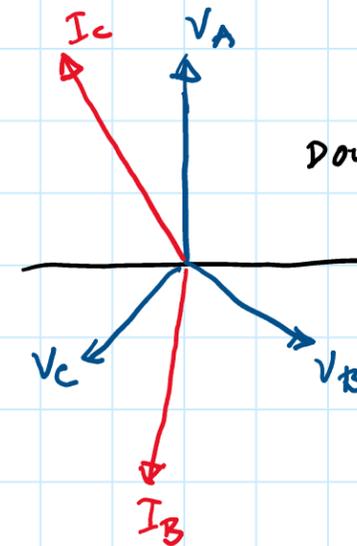


LINE-LINE FAULT

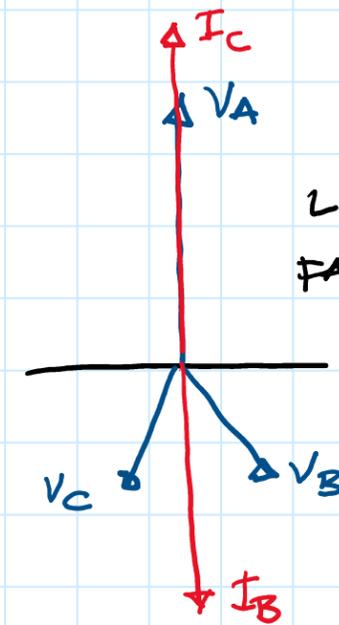


- ① Voltage decrease
- ② Current Increase
- ③ Phase angle b/w V and I increase

SEQUENCE VOLTAGE BEHAVIOR
DURING FAULTS

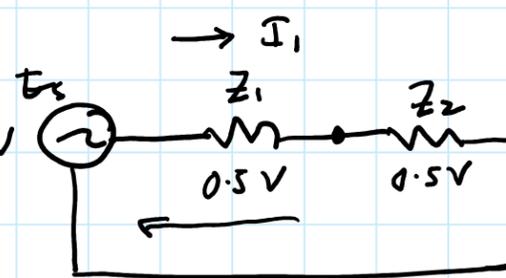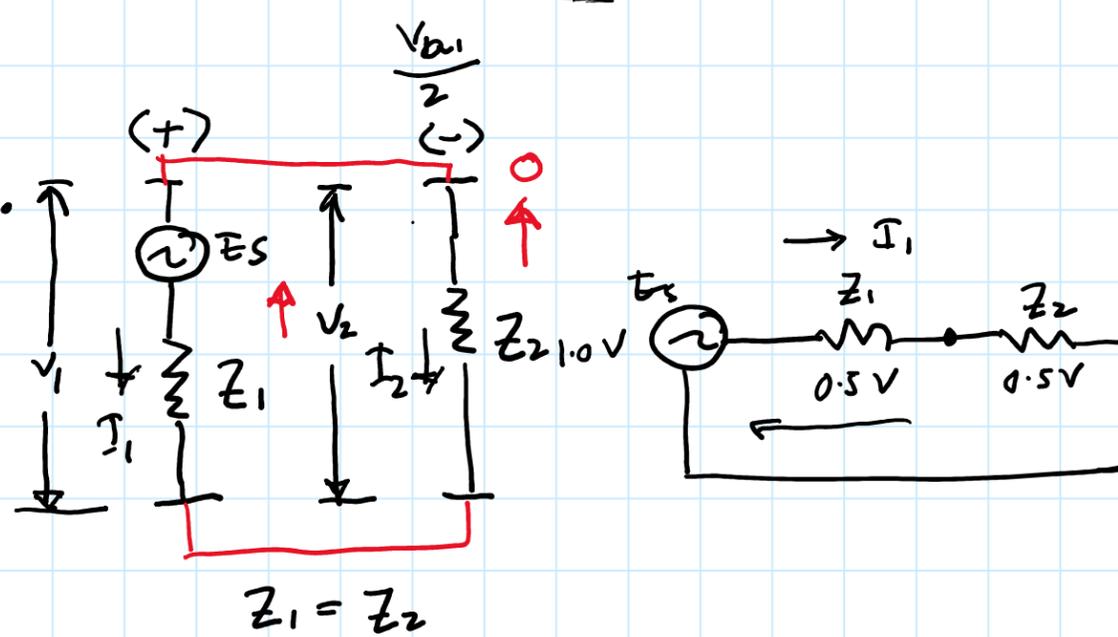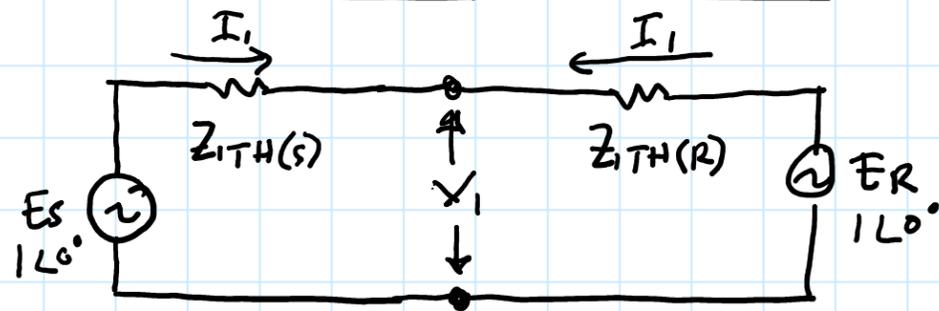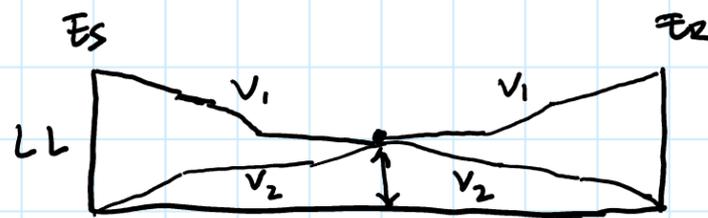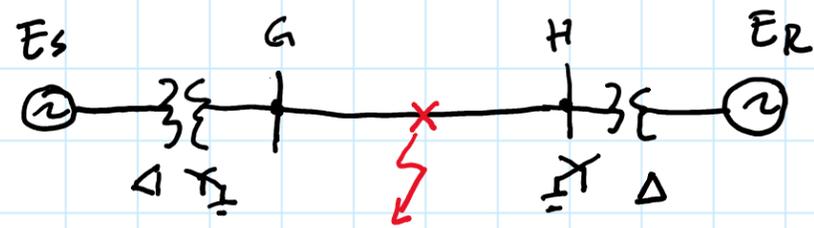

SERIES FAULT (ONE-PHASE OPEN)

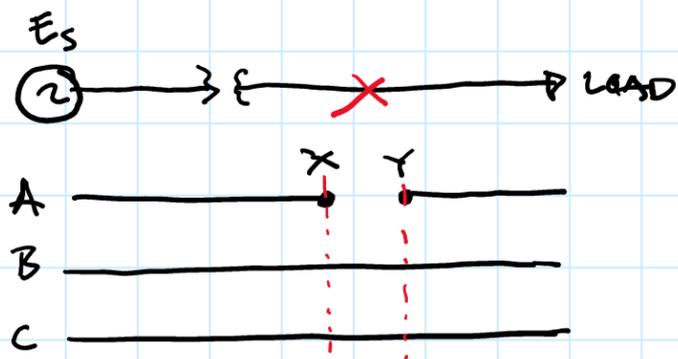

BOUNDARY CONDITIONS

$$I_A = 0 \quad \underline{V_{BXY}} = 0 \quad \underline{V_{CXY}} = 0$$


- ① $3V_0 = V_A + V_B + V_C$
 - ② $3V_1 = V_A + aV_B + a^2V_C$
 - ③ $3V_2 = V_A + a^2V_B + aV_C$
- } Phase A as Ref

$$3V_0 = V_A + \cancel{V_B} + \cancel{V_C}$$

$$3V_1 = V_A + \cancel{aV_B} + \cancel{a^2V_C}$$

$$3V_2 = V_A + \cancel{a^2V_B} + \cancel{aV_C}$$
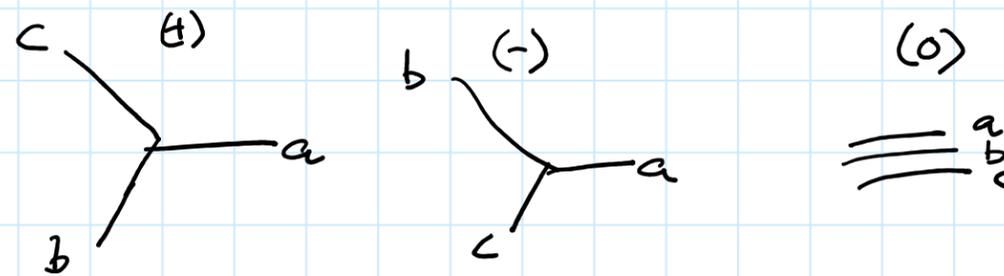
$$④ \quad 3V_0 = 3V_1 = 3V_2 = V_A \quad \rightarrow \quad V_0 = V_1 = V_2 = \frac{1}{3}V_A$$




Phase A as Ref



$$V_A = V_{a1} + V_{a2} + V_{a0} = V_1 + V_2 + V_0$$

$$V_B = V_{b1} + V_{b2} + V_{b0} = a^2V_1 + aV_2 + V_0 \quad a^2$$
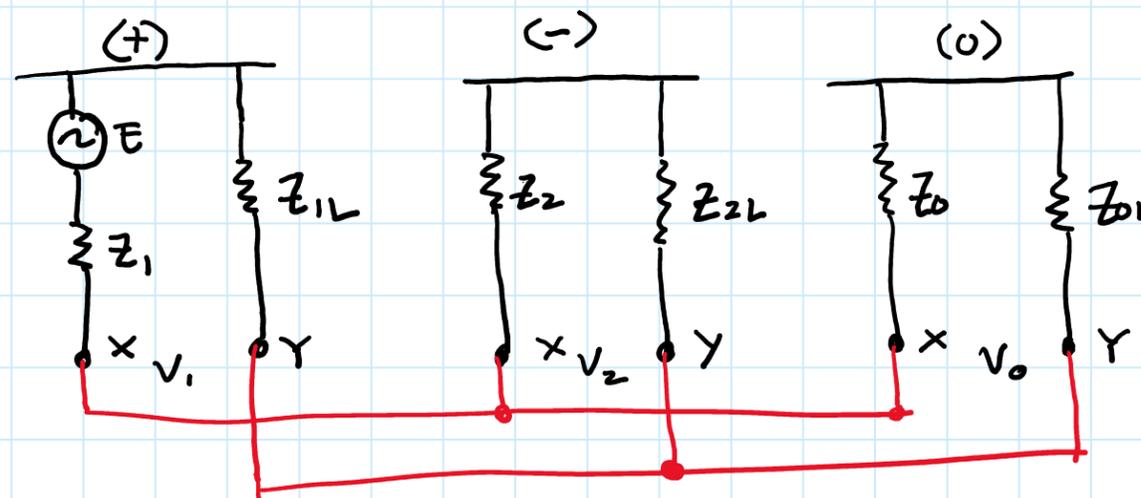
$$V_C = V_{c1} + V_{c2} + V_{c0} = aV_1 + a^2V_2 + V_0 \quad a$$



SERIES FAULT (ONE-PHASE OPEN)

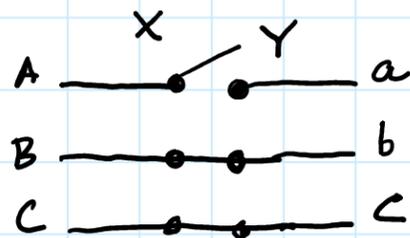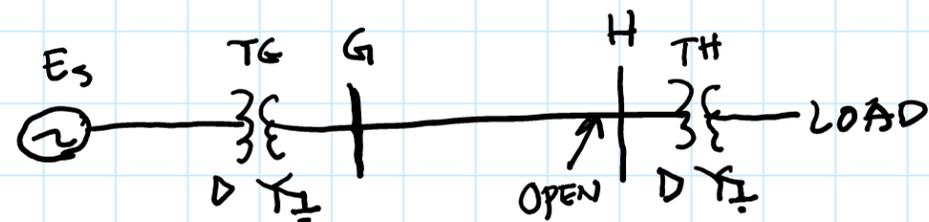

FOR WYE

$$I_{1G} = E_s / [Z_1 + Z_2 // Z_0]$$

$$I_{2G} = \frac{-I_{1G} \times Z_0}{Z_2 + Z_0}$$

$$I_{0G} = \frac{-I_{1G} \times Z_2}{Z_2 + Z_0}$$

ZERO SEQUENCE NETWORK IS NOT INCLUDED DUE TO OPENING @ BUS H

FOR DELTA




$$I_{1G} = -I_{2G} = E_s / (Z_1 + Z_2)$$

$$Z_1 = Z_{1TG} + Z_{1L} + Z_{1TH} + Z_{1LOAD} + Z_{1S}$$

$$Z_2 = Z_{2S} + Z_{2TG} + Z_{2L} + Z_{2TH} + Z_{2LOAD}$$

$$I_{0G} = 0$$

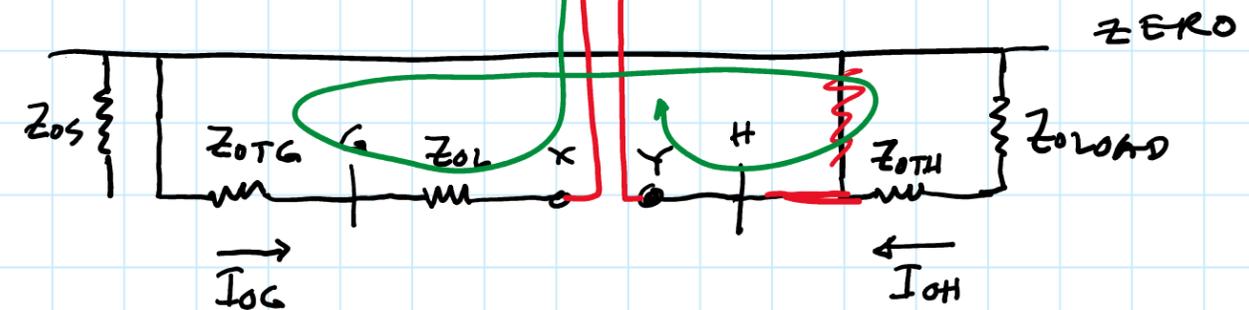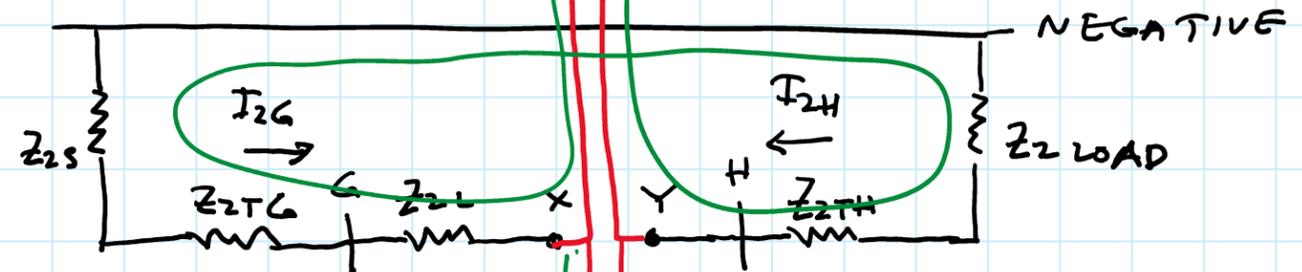
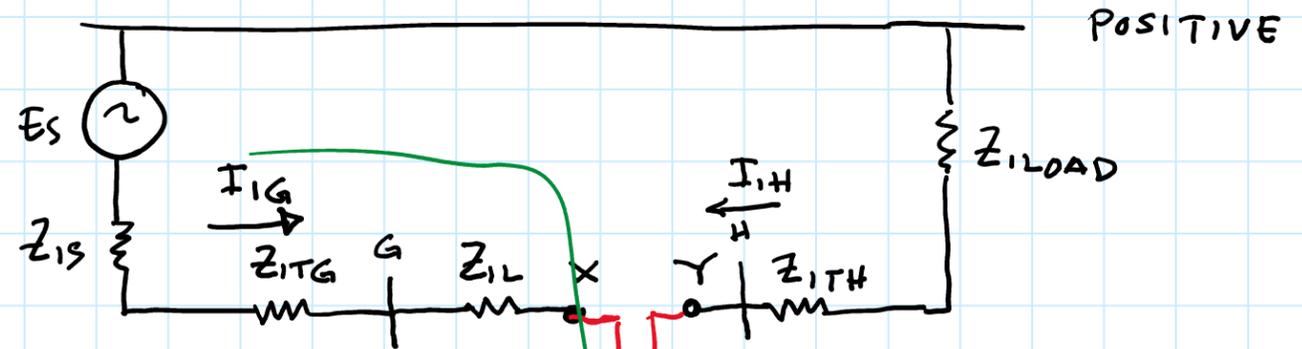
IF $Z_1 = Z_2$ THEN $I_{1G} = \frac{I_{PRE-FAULT}}{2}$



FOR DELTA: $I_2 = -I_1 \therefore \left| \frac{I_2}{I_1} \right| = 100\%$

FOR WYE: $I_2 = -I_1 \left(\frac{Z_0}{Z_2 + Z_0} \right) \therefore \left| \frac{I_2}{I_1} \right| \approx 50\% \text{ TO } 100\%$

SERIES FAULT (TWO-PHASES OPEN)

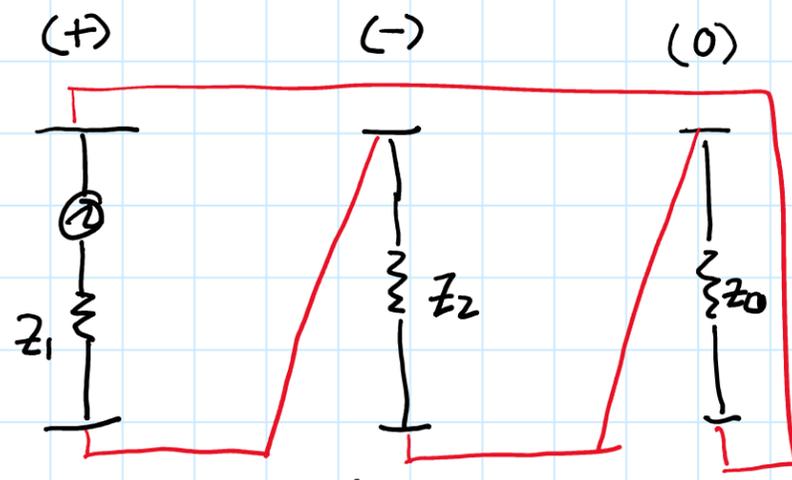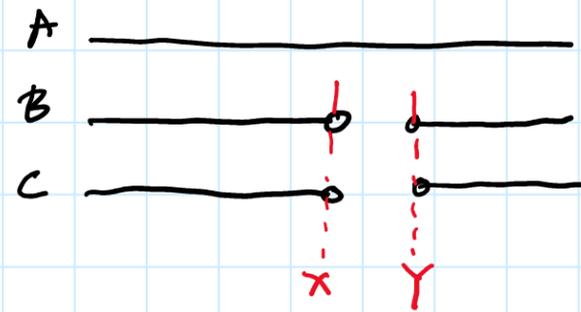

BOUNDARY CONDITIONS
 $I_B = 0$ $I_C = 0$ $V_{AXY} = 0$


$$3I_0 = I_A + I_B + I_C$$

$$3I_1 = I_A + aI_B + a^2I_C$$


$$3I_2 = I_A + a^2I_B + aI_C$$

$$3I_0 = 3I_1 = 3I_2 = I_A$$

$$I_0 = I_1 = I_2 = \frac{1}{3} I_A$$

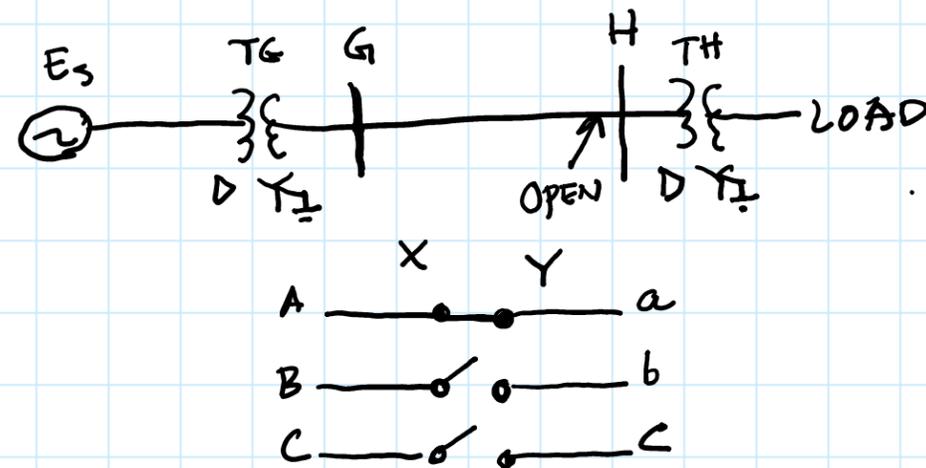

SERIES FAULT (TWO-PHASE OPEN)

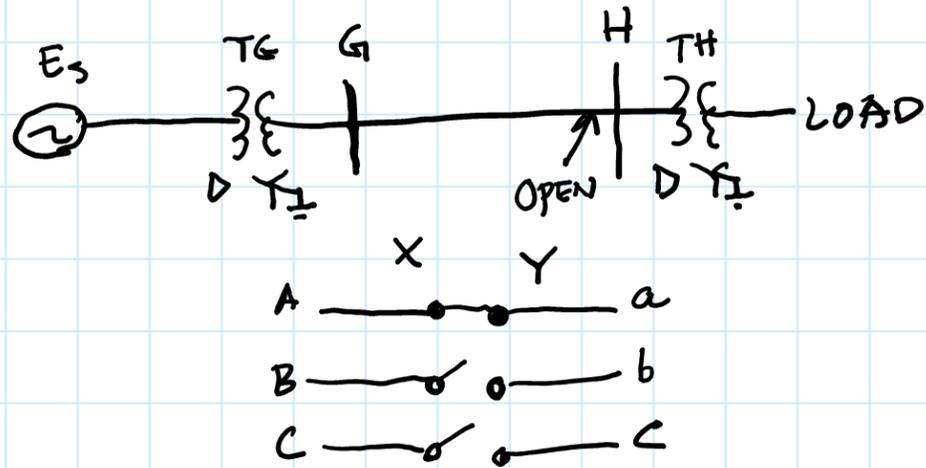

FOR DELTA

$$I_{1G} = I_{2G} = I_{0G} = 0 \quad Z_1 = Z_{1S} + Z_{1TG} + Z_{1L} + Z_{1TH} + Z_{1LOAD}$$


$$Z_2 = Z_{2S} + Z_{2TG} + Z_{2L} + Z_{2TH} + Z_{2LOAD}$$


$$\text{WYE} \rightarrow Z_0 = Z_{0TG} + Z_{0L} + Z_{0TH} + Z_{0LOAD}$$


FOR WYE

$$I_{1G} = I_{2G} = I_{0G}$$

$$I_{1G} = E_s / (Z_1 + Z_2 + Z_0)$$

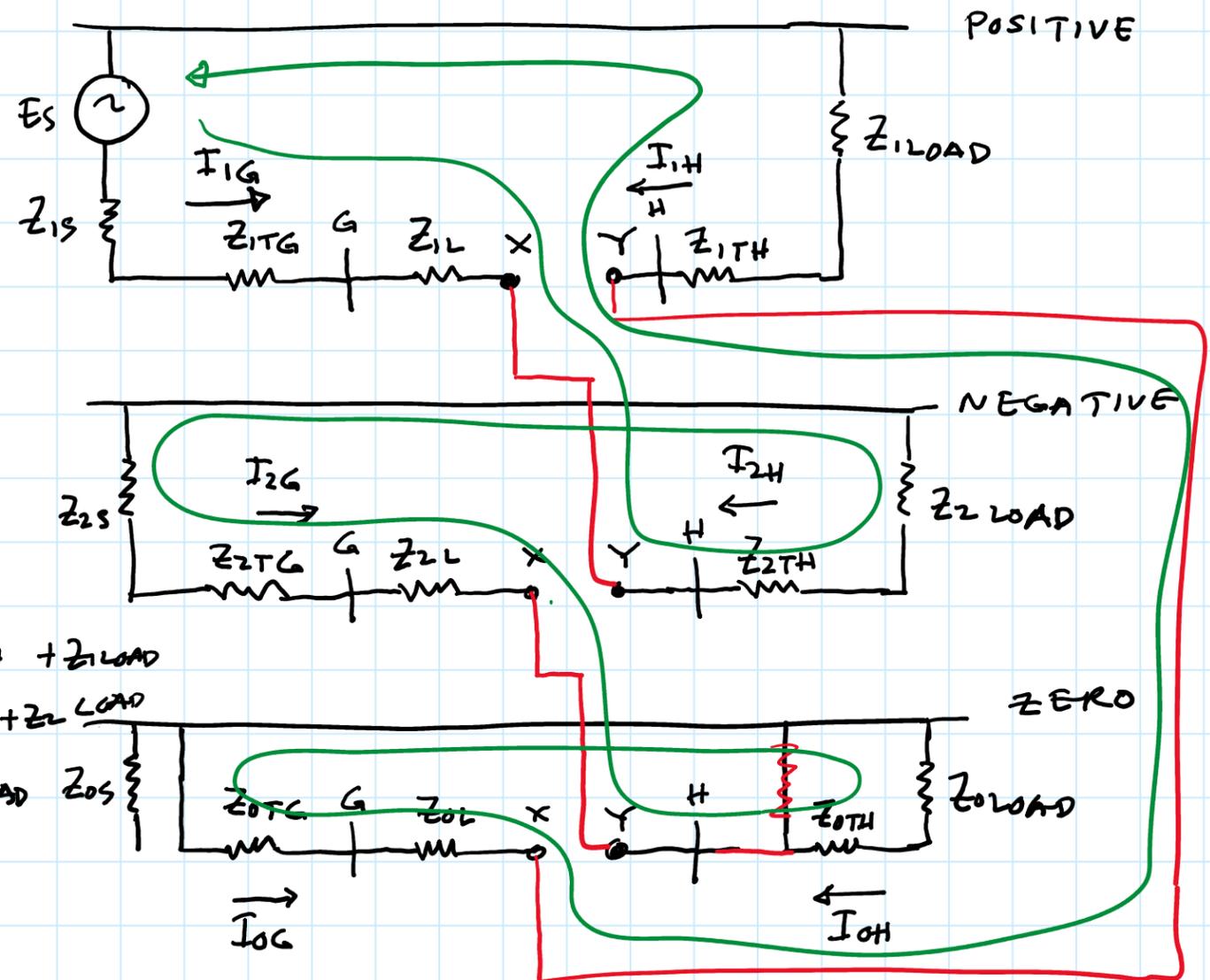

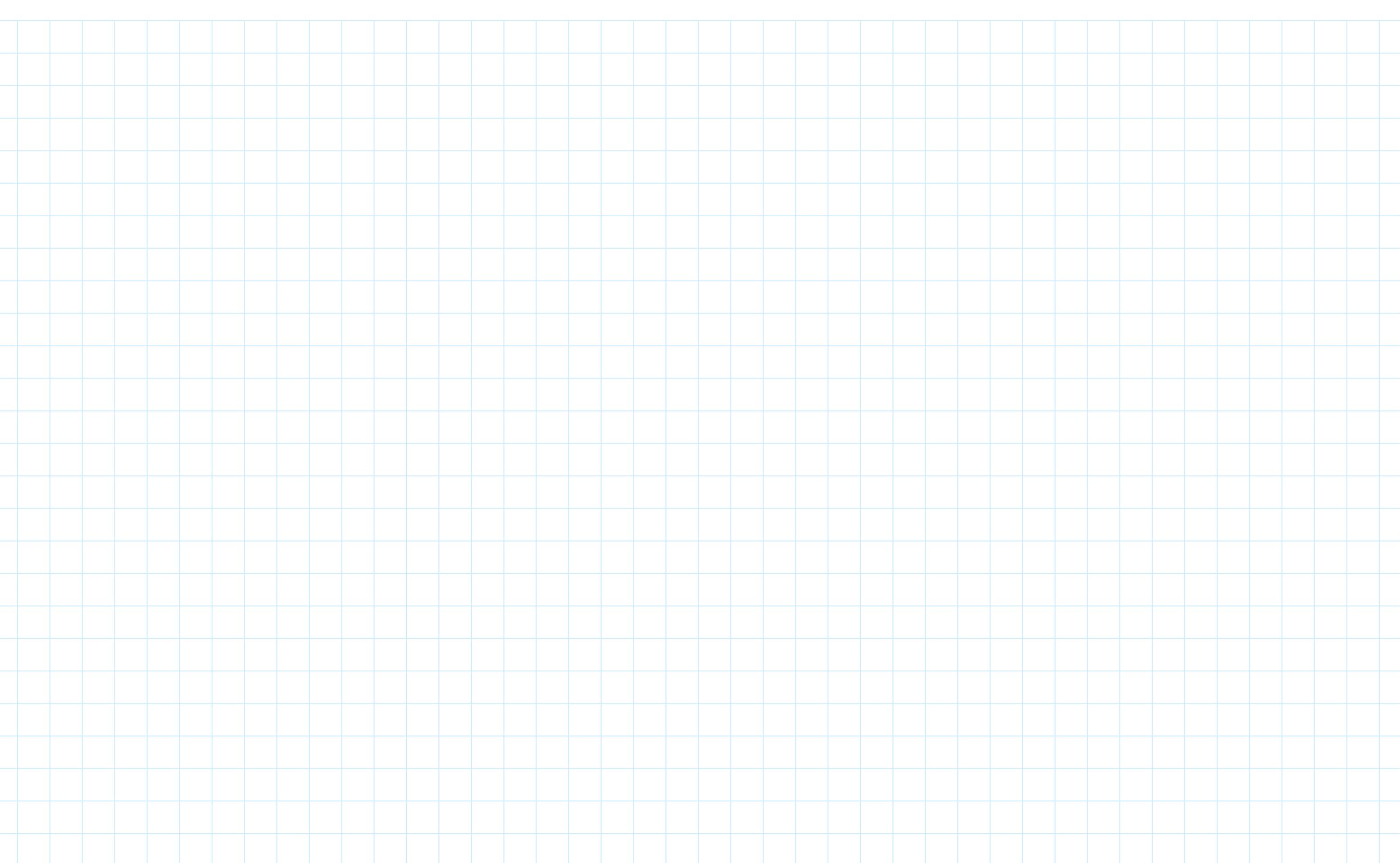

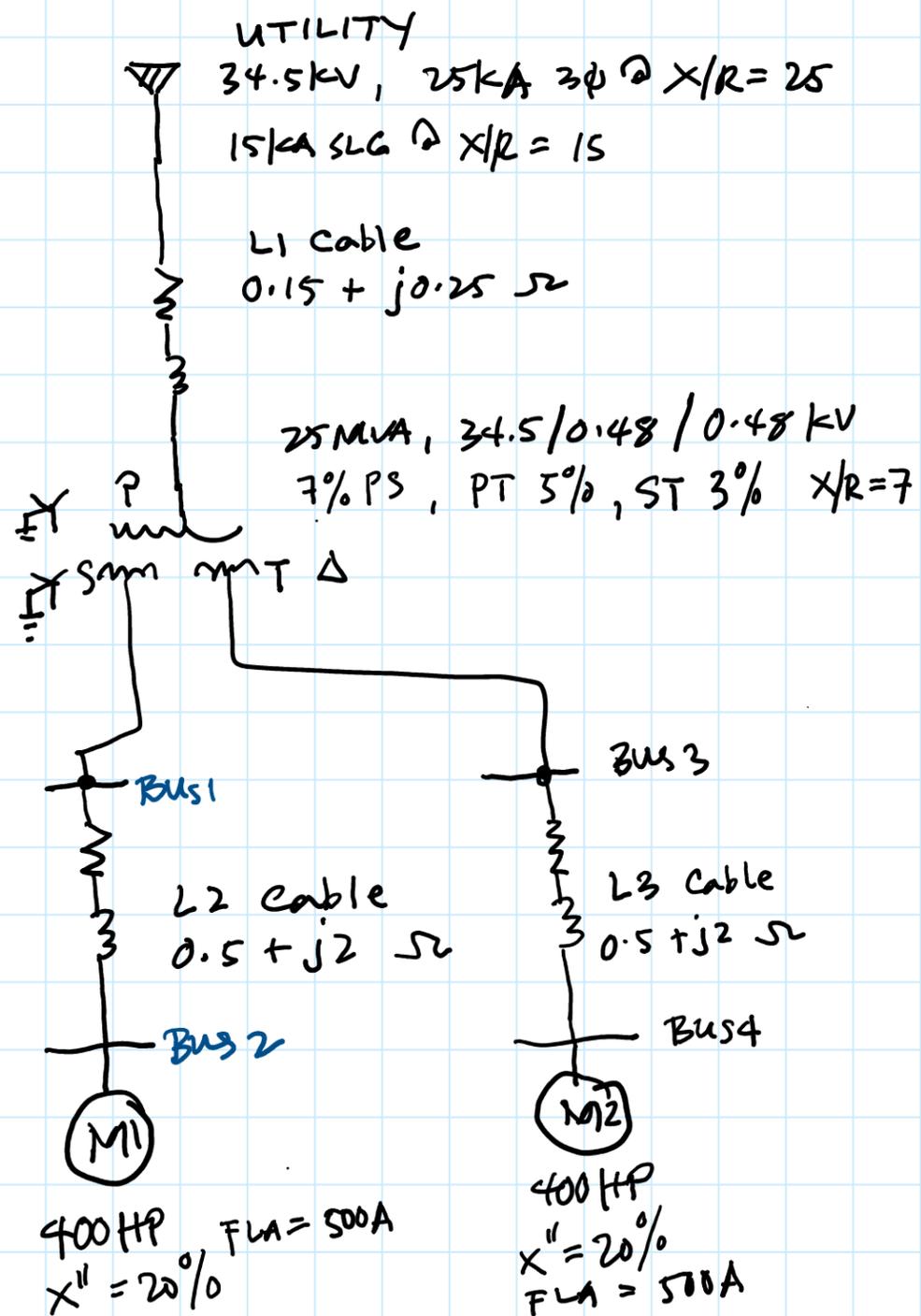

CHAPTER 5 ASSIGNMENT

- ① Using the same system that we used as example in Chapter 5 discussion, calculate for the momentary fault current at BUS1 if the fault types are:
 - A) Line to line fault
 - B) Single-line to ground fault
 - C) Double line to ground fault

- ② Also, draw the positive, negative and zero-sequence networks to aid in your calculations and analysis.

- ③ Calculate for the following 3-phase fault currents @ BUS1:
 - A) Interrupting current (1.5 to 4 cycle) using motor M1 and M2 transient reactance of $X' = 50\%$
 - B) Steady state fault current (≥ 30 cycle). Assume that all motor contributions have decayed to zero.