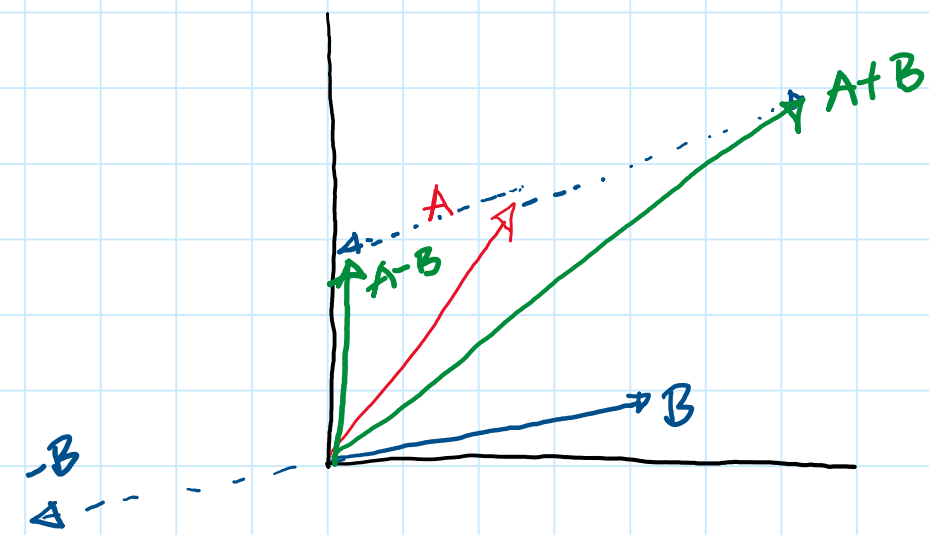


Phasor Operations



Tail to Tip addition

$$\bar{A} - \bar{B} = A + (-\bar{B})$$

$$\bar{A} = A \angle \alpha^\circ$$

$$\bar{B} = B \angle \beta^\circ$$

$$\bar{A}\bar{B} = AB \angle (\alpha + \beta)^\circ$$

$$\bar{A}^* = A \angle -\alpha^\circ \quad \bar{B}^* = B \angle -\beta^\circ$$

$$\bar{A}\bar{A}^* = AA \angle (\alpha - \alpha)^\circ = A^2$$

$$\frac{\bar{A}}{\bar{B}} = \frac{A}{B} \angle (\alpha - \beta)^\circ$$

Per Unit Method


Per Unit Quantity = actual quantity / base quantity

Actual quantities can be scalar or complex

Percent Quantity = per unit $\times 100\%$

STEP ① Select the three-phase base power (S_b) and the phase-to-phase base voltage (V_b) values. Base power is the same for the whole system. Base voltage needs to be adjusted when crossing transformers according to transformer ratio


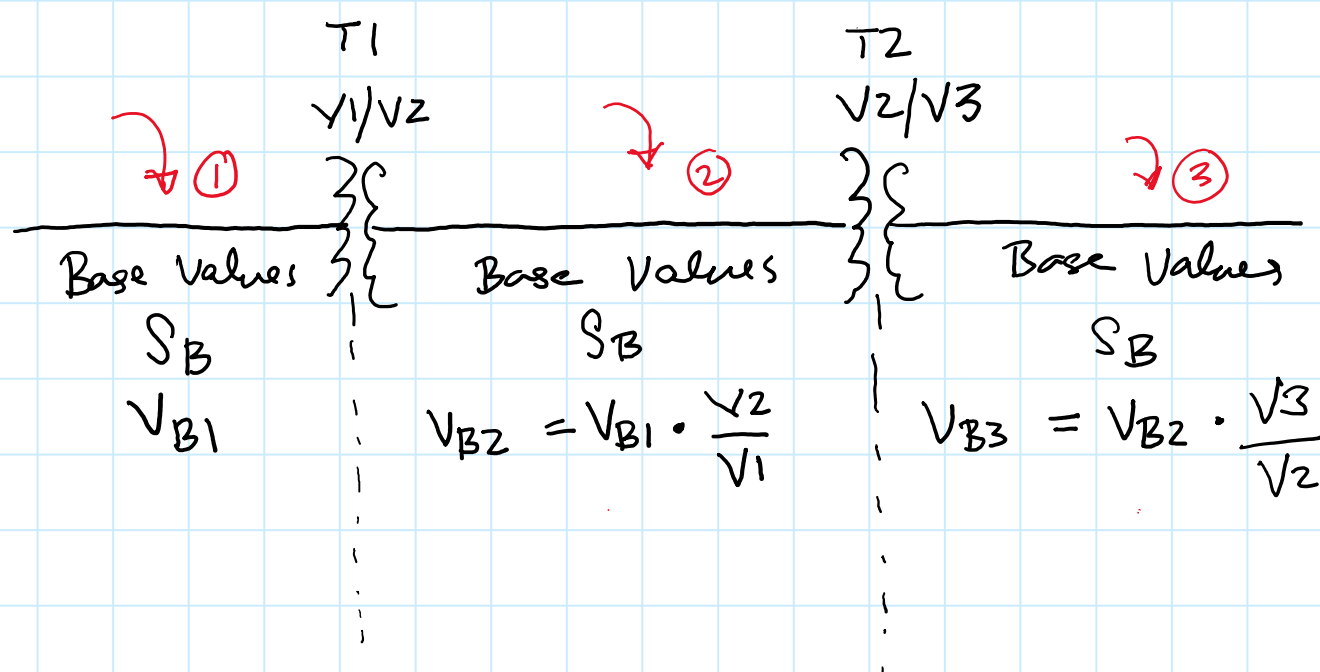
STEP ② Calculate base current (I_b) and base impedance (Z_b) for each voltage level.



$n = 1, 2, 3, \text{etc.}$

$$I_{Bn} = \frac{S_B}{\sqrt{3} V_{Bn}}$$
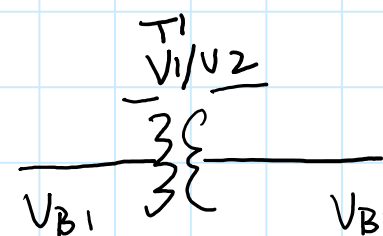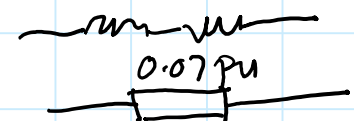
$$Z_{Bn} = \frac{V_{Bn} / \sqrt{3}}{I_{Bn}} = \frac{V_{Bn}^2}{S_B}$$



$$V_{B1} = V_1$$


$$V_{B2} = V_2$$

$$V_{B2} = V_{B1} \cdot \frac{V_2}{V_1}$$

$$V_{B1}(pu) = \frac{V_{B1}}{V_{B1}} = 1 pu$$

$$V_{B2}(pu) = \frac{V_{B2}}{V_{B2}} = 1 pu$$

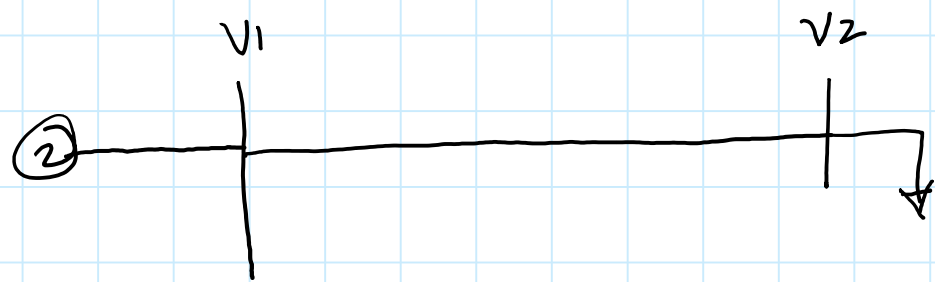Example power flow on 69kV Transmission Line



$$S = P + jQ$$

Sending End

$$V_1 = 74.29 \angle 6.05^\circ \text{ kV} \quad \bar{S} = 62.65 + j58.26 \text{ MVA}$$

$$\text{Base Voltage} = 69 \text{ kV}$$

$$\text{Base Power} = 100 \text{ MVA}$$

$$V_1 = \frac{74.29 \angle 6.05^\circ \text{ kV}}{69 \text{ kV}} = 1.077 \text{ pu}$$

$$S = \frac{62.65 + j58.26 \text{ MVA}}{100 \text{ MVA}} = 0.6265 + j0.5826 \text{ pu}$$

Changing Base

$$Z_{PU}^{OLD} = \frac{Z}{Z_{BASE}^{OLD}} = Z \cdot \frac{S_{BASE}^{OLD}}{(V_{BASE}^{OLD})^2}$$


$$Z_{PU}^{NEW} = \frac{Z}{Z_{BASE}^{NEW}} = Z \cdot \frac{S_{BASE}^{NEW}}{(V_{BASE}^{NEW})^2}$$

$$Z_{PU}^{NEW} = Z_{PU}^{OLD} \cdot \frac{S_{BASE}^{NEW}}{S_{BASE}^{OLD}} \cdot \left(\frac{V_{BASE}^{OLD}}{V_{BASE}^{NEW}} \right)^2$$

$$Z_{PU}^{NEW} = Z \cdot \frac{S_{BASE}^{NEW}}{(V_{BASE}^{NEW})^2}$$

$$Z = Z_{PU}^{OLD} \cdot \frac{(V_{BASE}^{OLD})^2}{S_{BASE}^{OLD}}$$

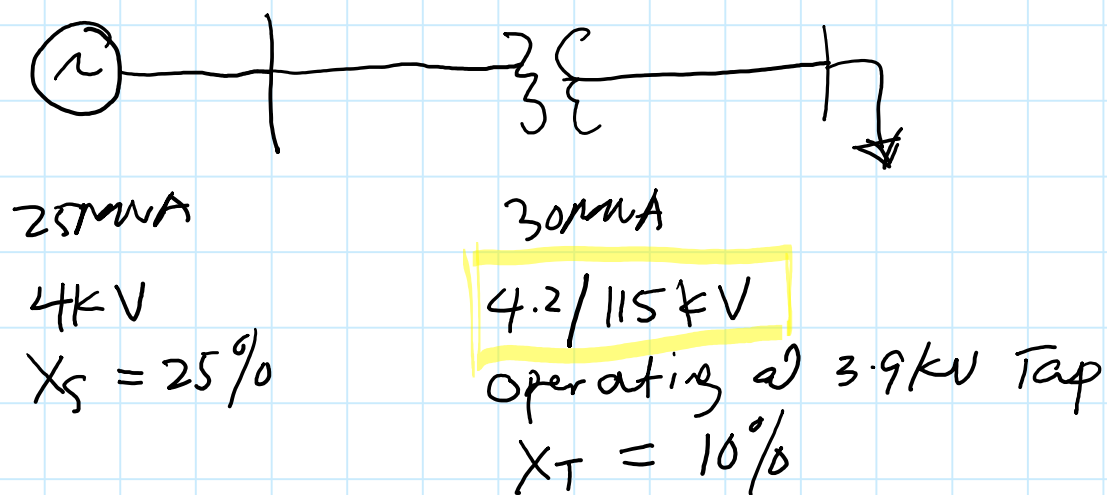EXAMPLE: Using 100MVA base, 110kV base (high-side), find the following in per unit



$$S_B = 100 MVA$$

$$V_{BASE H} = \underline{110 kV}$$

$$\frac{V_{BASE L}}{V_{BASE H}} = \frac{V_L}{V_H}$$

$$\frac{V_{BASE L}}{110 kV} = \frac{3.9 kV}{115 kV}$$

$$V_{BASE L} = 3.9 \times 110 / 115$$

$$= \underline{3.73 kV}$$

$$X_G = \frac{25}{100} \left(\frac{100}{25} \right) \left(\frac{4 kV}{3.73 kV} \right)^2 = 1.15 pu$$

$$X_{TH} = \frac{10}{100} \left(\frac{100}{30} \right) \left(\frac{115 kV}{110 kV} \right)^2 = 0.3643 pu$$

$$X_{TL} = \frac{10}{100} \left(\frac{100}{30} \right) \left(\frac{3.9}{3.73} \right)^2 = 0.3643 pu$$

