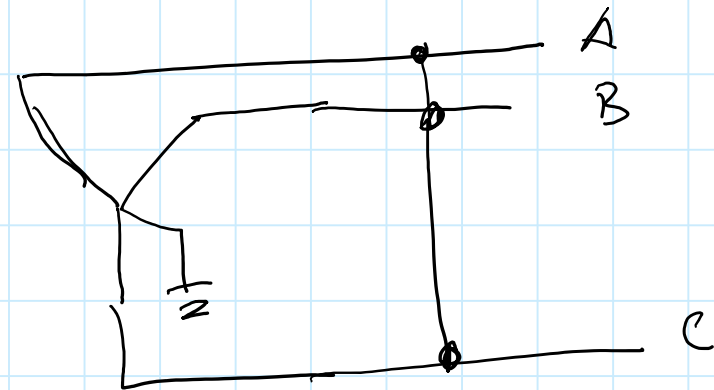



Fault Analysis Using Symmetrical Components

Method to Calculate Unbalanced Short Circuits

- ① Determine the simulation points
- ② Find system sequence network
- ③ Calculate Thevenin equivalent
- ④ Connect sequence networks and calculate fault current
- ⑤ Calculate sequence voltages and currents
- ⑥ Calculate phase quantities



Three Phase Fault

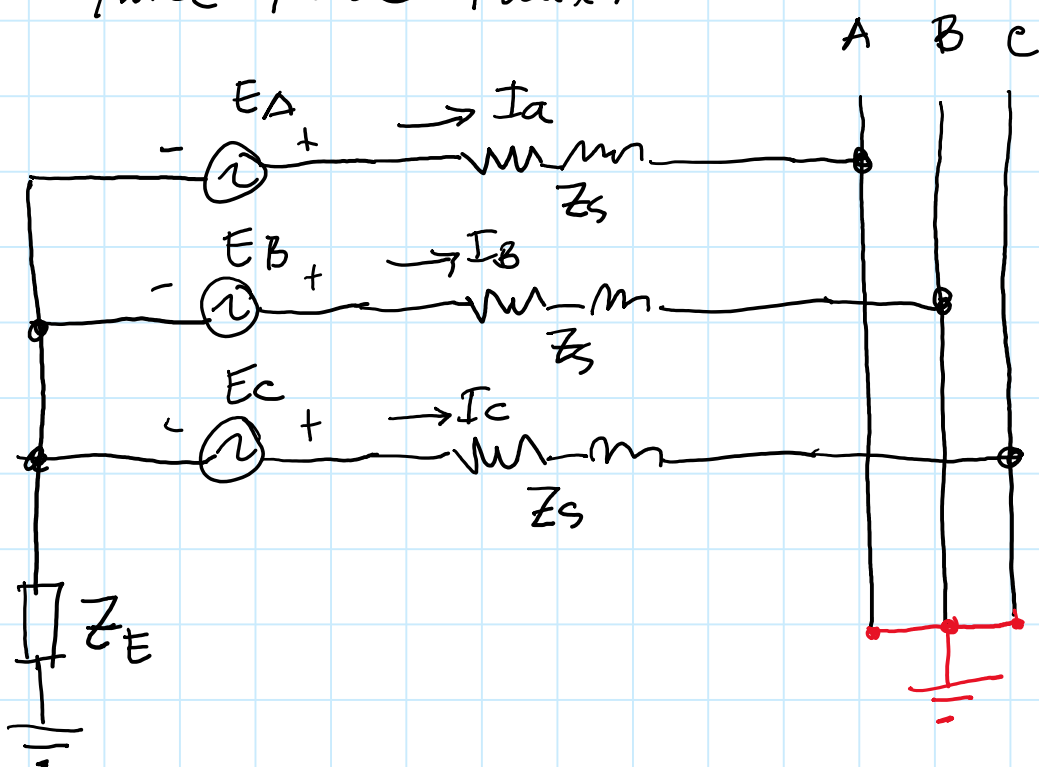

$$I_A = I_0 + I_1 + I_2 \quad (1)$$

$$I_B = I_0 + a^2 I_1 + a I_2 \quad (2)$$

$$I_C = I_0 + a I_1 + a^2 I_2 \quad (3)$$

$$3I_0 = I_A + I_B + I_C \quad (4)$$

$$3I_1 = I_A + a I_B + a^2 I_C \quad (5)$$

$$3I_2 = I_A + a^2 I_B + a I_C \quad (6)$$

From eq (4)

$$3I_0 = I_A + I_B + I_C = 0 \quad ; \quad \boxed{I_0 = 0}$$

From eq (5)

$$3I_1 = I_A + a I_B + a^2 I_C = I_A + a [a^2 I_A] + a^2 [a I_A]$$

$$3I_1 = I_A + a^3 I_A + a^3 I_A = 3I_A$$

$$\boxed{I_1 = I_A}$$

$$a^3 \cdot a =$$

From eq (6)

$$3I_2 = I_A + a^2 I_B + a I_C = I_A + a^2 [a^2 I_A] + a [a I_A]$$

$$= I_A + a^4 I_A + a^2 I_A$$

$$= I_A + a I_A + a^2 I_A$$

$$= I_A (1 + a + a^2)$$


$$3I_2 = 0$$

$$\boxed{I_2 = 0}$$

BOUNDARY CONDITIONS


$$I_A + I_B + I_C = 0 \quad \checkmark$$

$$V_A = V_B = V_C = 0$$

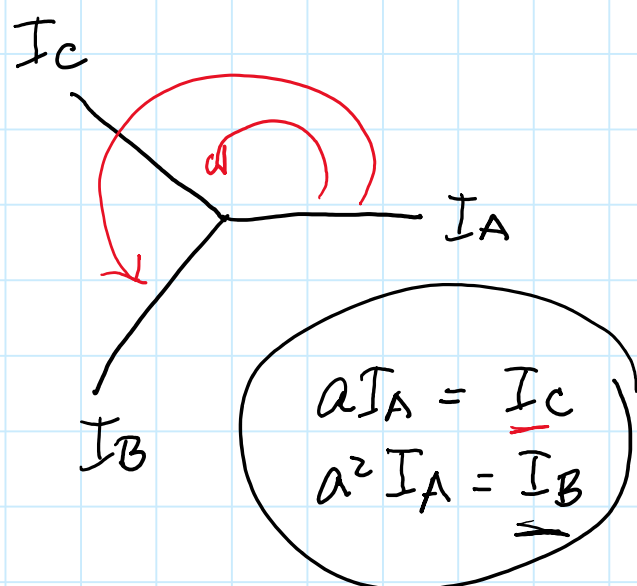

CONCLUSION: For Three-Phase Fault, there are no zero and negative sequence currents present.

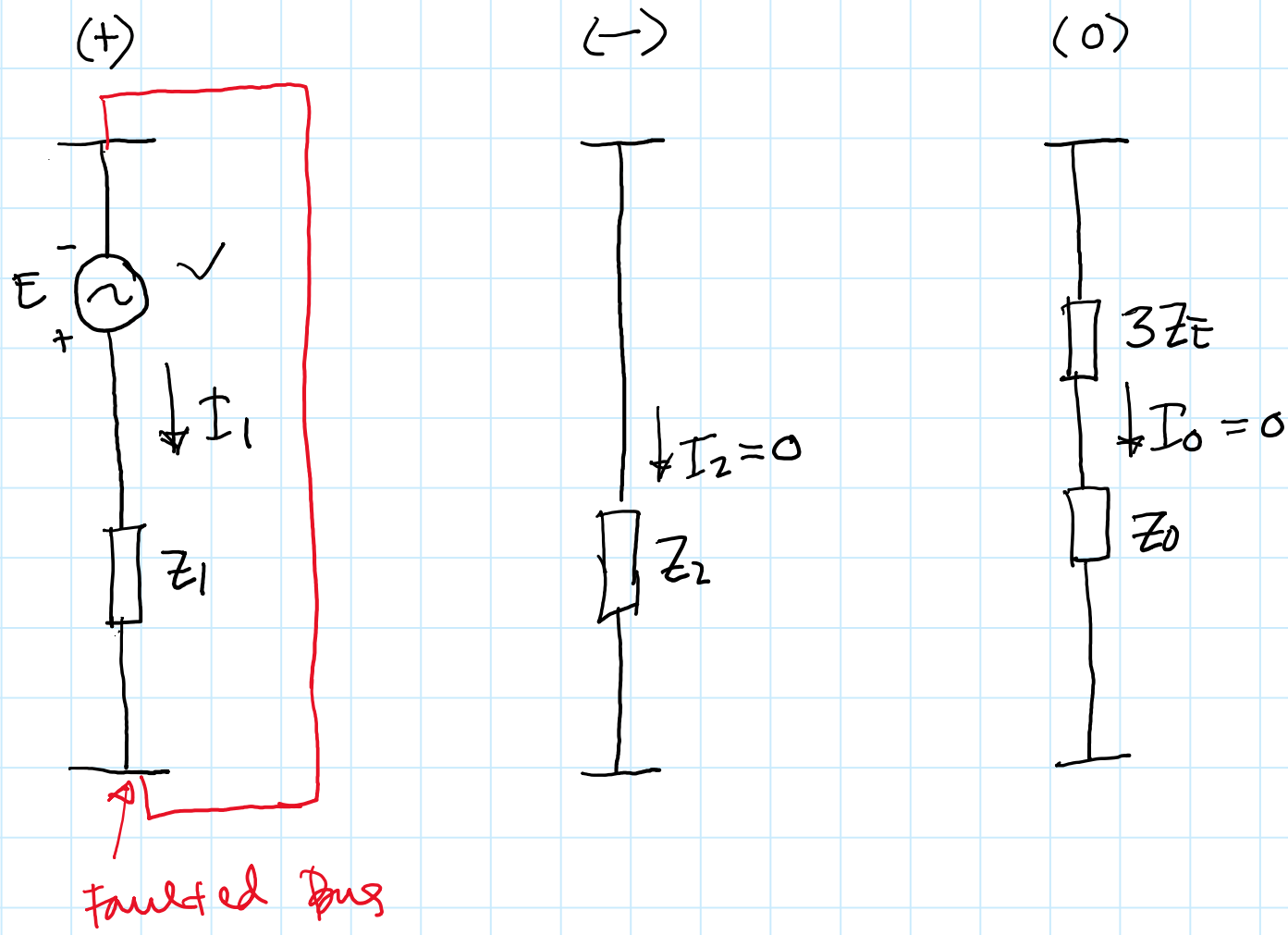
SEQUENCE NETWORK CONNECTION (THREE PHASE FAULT)



FAULT CURRENTS:

$$I_A = I_1 = \frac{E}{Z_1} ; I_B = a^2 I_A ; I_C = a I_A$$

Phase To Phase Fault

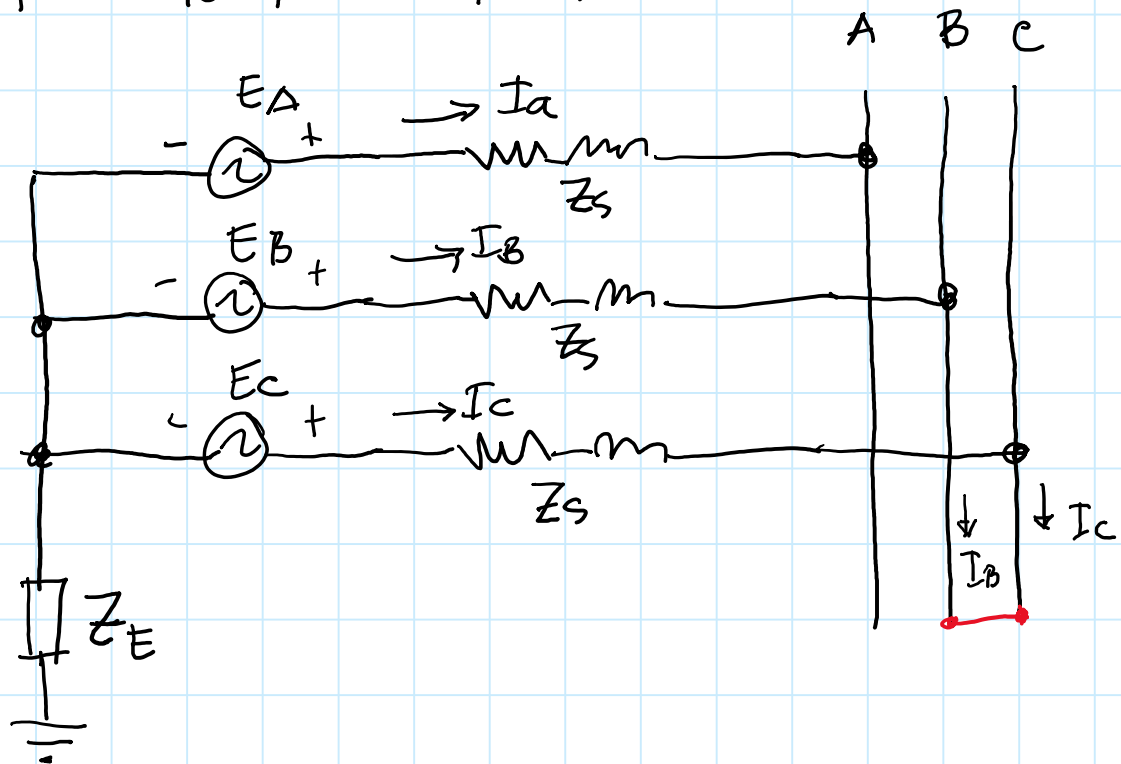

$$I_A = I_0 + I_1 + I_2 \quad (1)$$

$$I_B = I_0 + a^2 I_1 + a I_2 \quad (2)$$

$$I_C = I_0 + a I_1 + a^2 I_2 \quad (3)$$

$$3I_0 = I_A + I_B + I_C \quad (4)$$

$$3I_1 = I_A + a I_B + a^2 I_C \quad (5)$$

$$3I_2 = I_A + a^2 I_B + a I_C \quad (6)$$

BOUNDARY CONDITIONS:

$$V_B = V_C ; I_B = -I_C ; I_A = 0$$

FROM EQ (4)

$$3I_0 = I_A + I_B + I_C = 0 + I_B + (-I_B) = 0$$

$$I_0 = 0$$

FROM EQ (5)

$$3I_1 = I_A + a I_B + a^2 I_C = 0 + a I_B + a^2 (-I_B)$$

$$\checkmark 3I_1 = (a - a^2) I_B = (\sqrt{3} \angle 90^\circ) I_B$$

$$I_1 = \left(\frac{\sqrt{3} \angle 90^\circ}{3} \right) I_B = \left(\frac{1 \angle 90^\circ}{\sqrt{3}} \right) I_B$$

FROM EQ (6)

$$3I_2 = I_A + a^2 I_B + a I_C = 0 + a^2 I_B + a (-I_B)$$

$$\checkmark 3I_2 = (a^2 - a) I_B = (\sqrt{3} \angle -90^\circ) I_B$$

$$I_1 = -I_2 \quad \text{FROM EQ (5) AND (6)}$$

$$|I_2| / |I_1| = 1$$

$$I_B = a^2 I_1 + a I_2 = (a^2 - a) I_1$$


$$= (a^2 - a) \left[\frac{E}{Z_1 + Z_2} \right]$$

$$= (\sqrt{3} \angle 90^\circ) \frac{E}{2 Z_1}$$

$$= \left(\frac{\sqrt{3} \angle 90^\circ}{2} \right) \left(\frac{E}{Z_1} \right) \quad 3\phi$$


$$I_{LL} = 0.866 I_{3\phi}$$

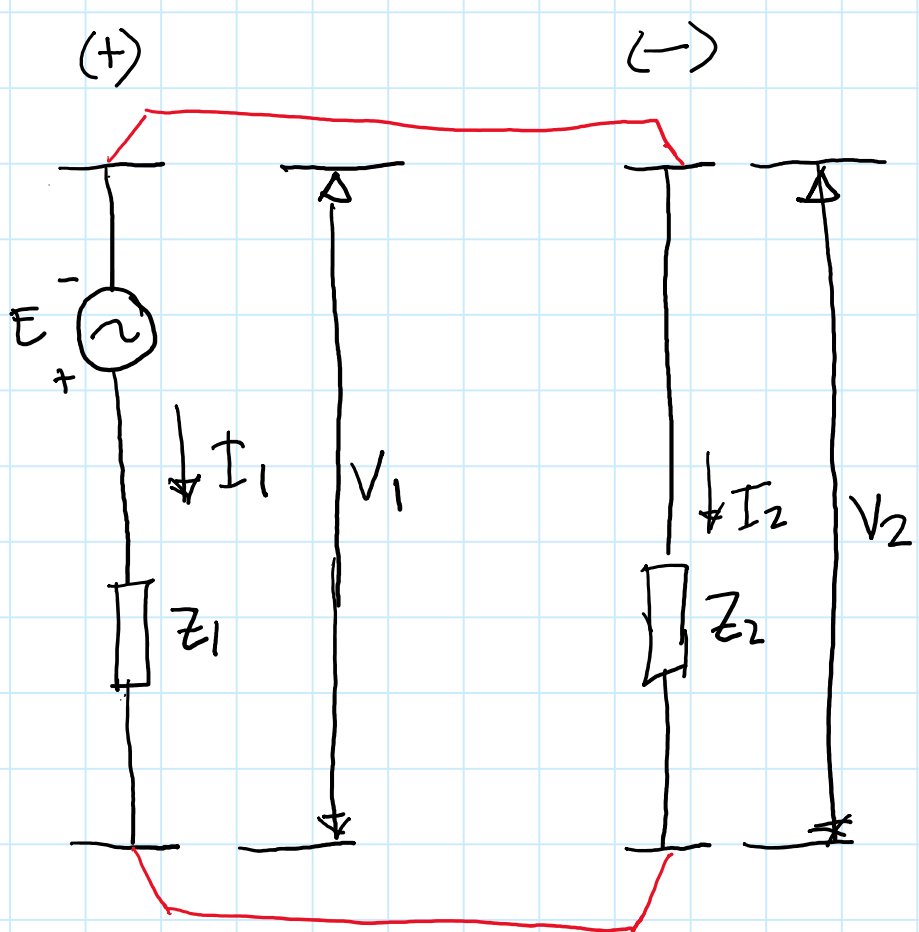SEQUENCE NETWORK CONNECTIONS (LINE TO LINE FAULT)



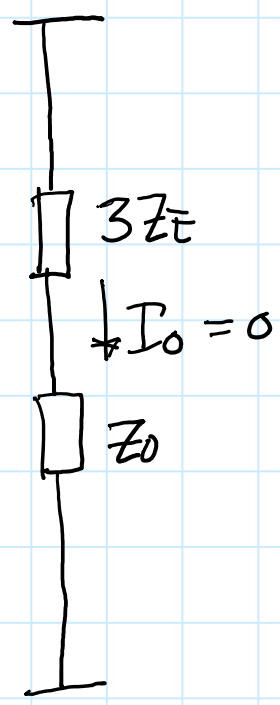(0)


CONCLUSION: There is no zero-sequence current present in a line to line fault.





$$I_1 = \frac{E}{Z_1 + Z_2} = -I_2 = \frac{E}{2(Z_1)}$$

$$V_1 = V_2$$

$$E = I_1 Z_1 + V_1$$



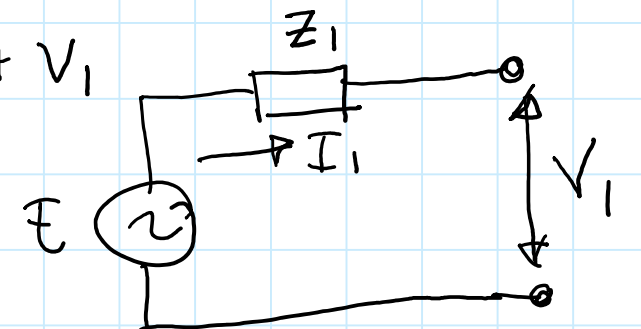


Phase To Phase Fault (Phasors)

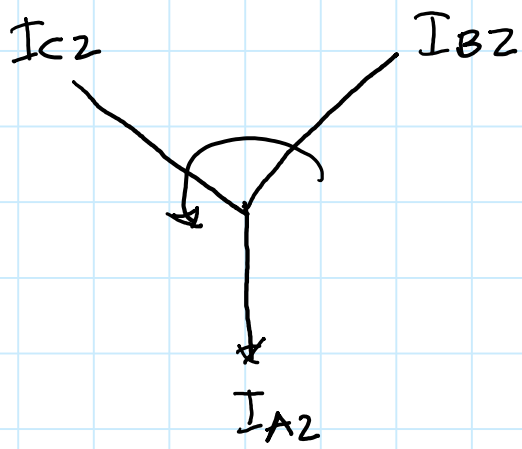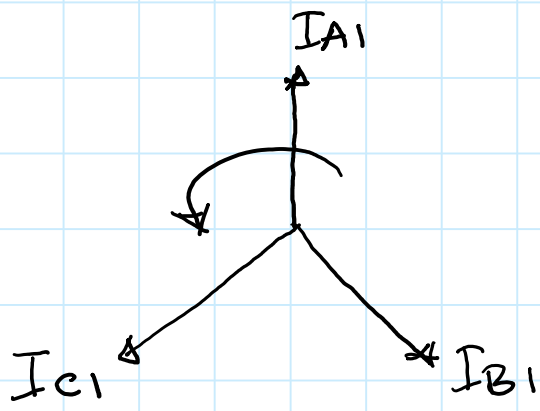

NO ZERO SEQUENCE

$$I_1 = -I_2$$

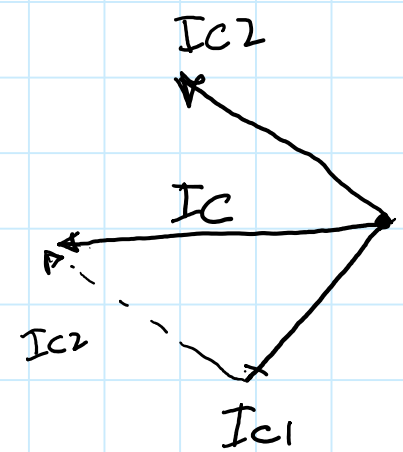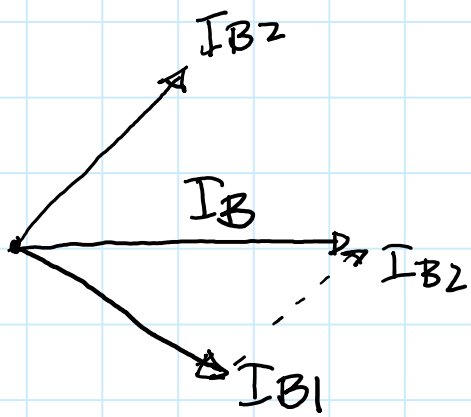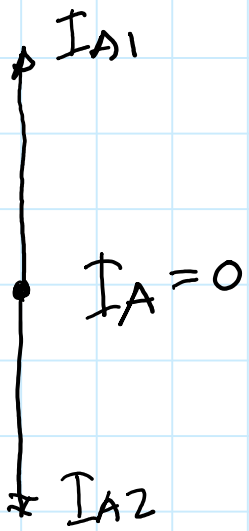

$$I_A = I_{A1} + I_{A2} + \cancel{I_{A0}}^{\rightarrow 0}$$


$$I_B = I_{B1} + I_{B2} + \cancel{I_{B0}}^{\rightarrow 0}$$

$$I_C = I_{C1} + I_{C2} + \cancel{I_{C0}}^{\rightarrow 0}$$

$$I_B = \sqrt{3} |I_{B1}|$$

$$I_C = \sqrt{3} |I_{C1}|$$

SINGLE LING TO GROUND FAULT

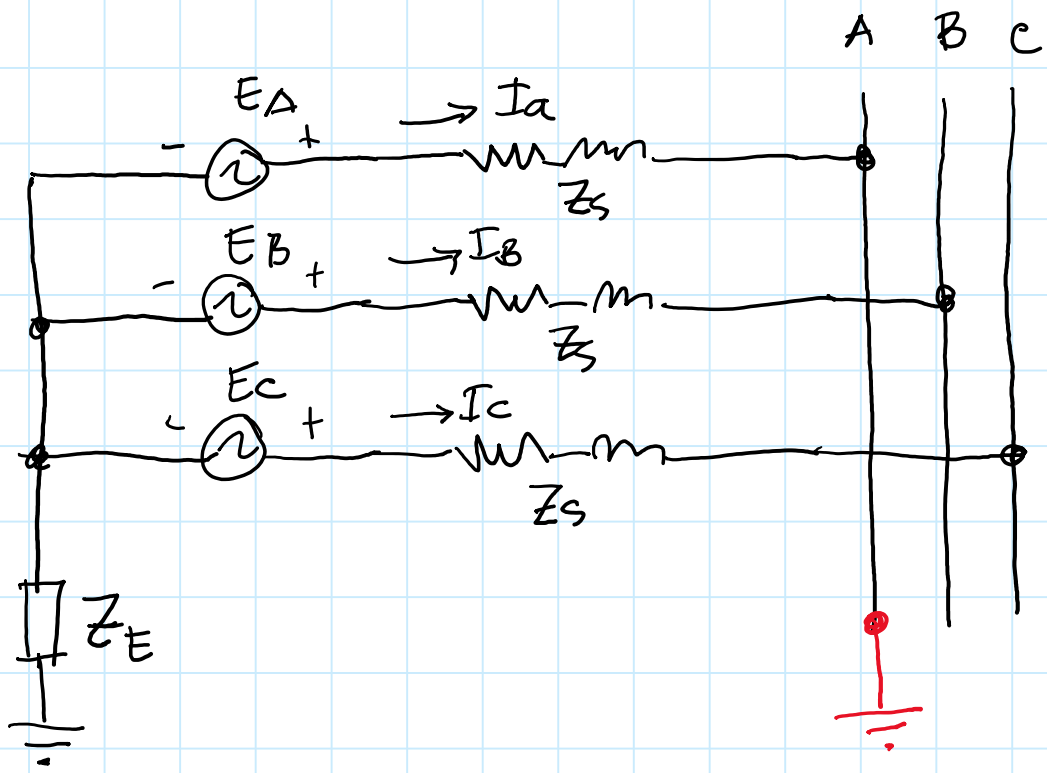

BOUNDARY CONDITIONS:

$$V_A = 0 ; \underline{I_B = I_C = 0}$$

$$I_A = I_0 + I_1 + I_2 \quad (1)$$

$$I_B = I_0 + a^2 I_1 + a I_2 \quad (2)$$

$$I_C = I_0 + a I_1 + a^2 I_2 \quad (3)$$

$$3I_0 = I_A + I_B + I_C \quad (4)$$

$$3I_1 = I_A + a I_B + a^2 I_C \quad (5)$$

$$3I_2 = I_A + a^2 I_B + a I_C \quad (6)$$

FROM EQ (4)

$$3I_0 = I_A + \cancel{I_B} + \cancel{I_C} = I_A$$

$$\boxed{3I_0 = I_A}$$

FROM EQ (5)

$$3I_1 = I_A + a \cancel{I_B} + a^2 \cancel{I_C}$$

$$\boxed{3I_1 = I_A}$$

FROM EQ (6)


$$3I_2 = I_A + a^2 \cancel{I_B} + a \cancel{I_C}$$

$$\boxed{3I_2 = I_A}$$

FROM EQ (4), (5) & (6)

$$\sqrt{I_A = 3I_1 = 3I_2 = 3I_0} ; \boxed{I_1 = I_2 = I_0 = \frac{1}{3} I_A}$$


$$I_0 / I_1 = 1$$

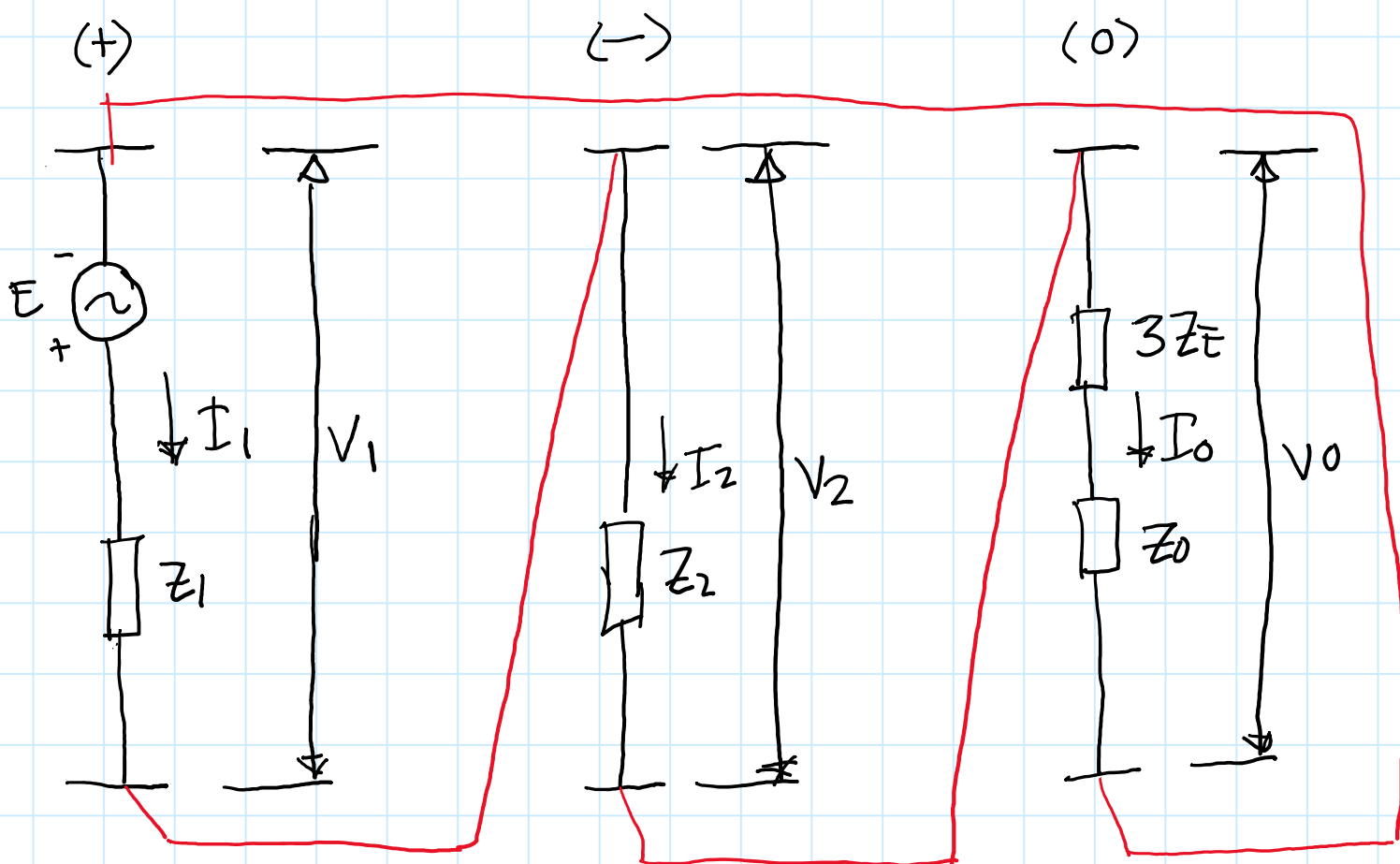

$$I_0 = \frac{E}{Z_1 + Z_2 + Z_0 + 3Z_E}$$

$$I_A = 3I_0 = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_E}$$

SEQUENCE IMPEDANCE OF A GENERATOR

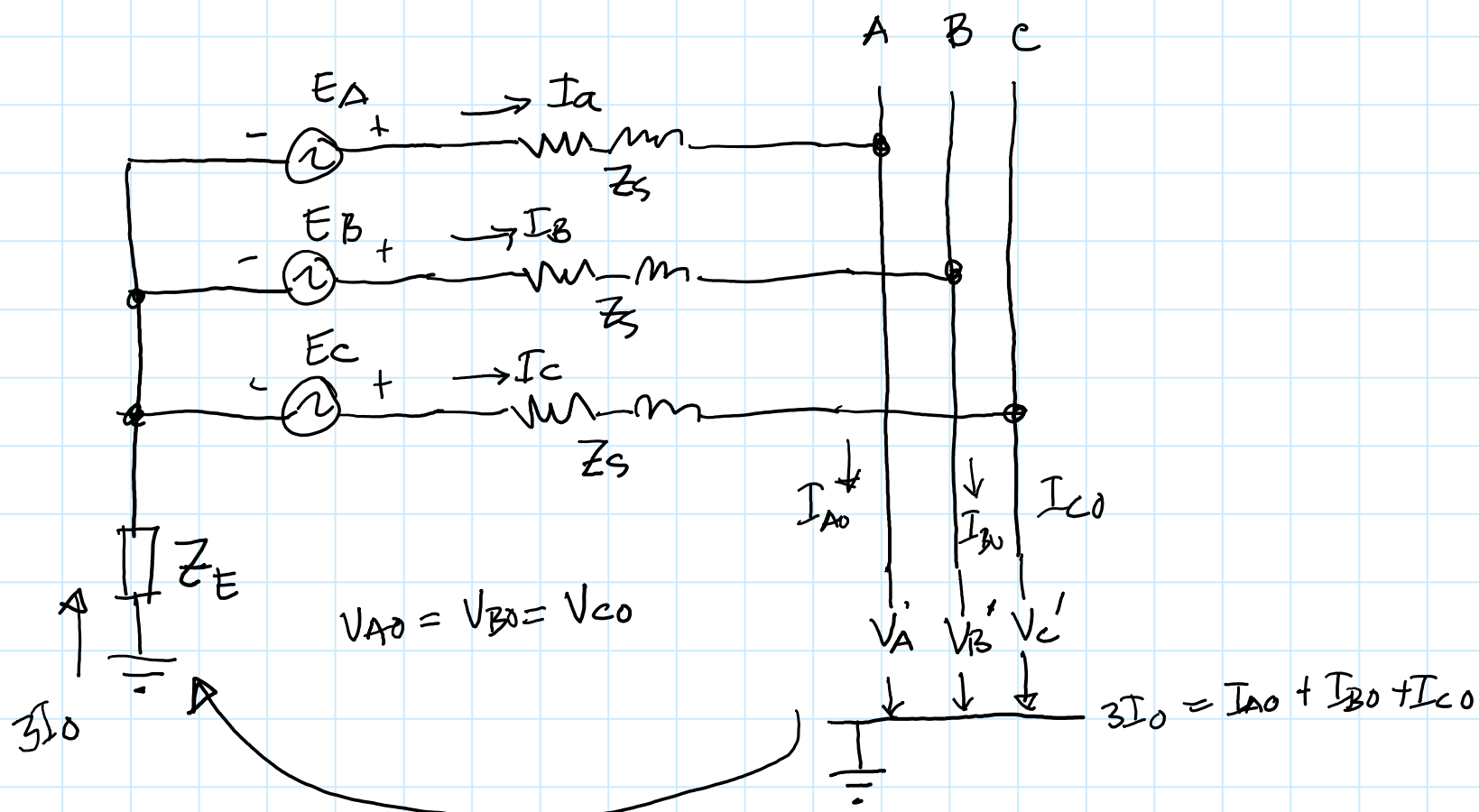


$$E_A = Z_s I_A + Z_M I_B + Z_M I_C + V_A$$

$$E_B = Z_M I_A + Z_s I_B + Z_M I_C + V_B$$


$$E_C = Z_M I_A + Z_M I_B + Z_s I_C + V_C$$

POS SEQ NETWORK

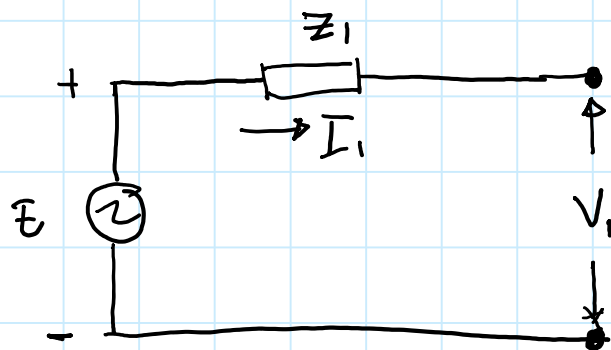


$$E = I_1 Z_1 + V_1$$

NEG SEQ NETWORK

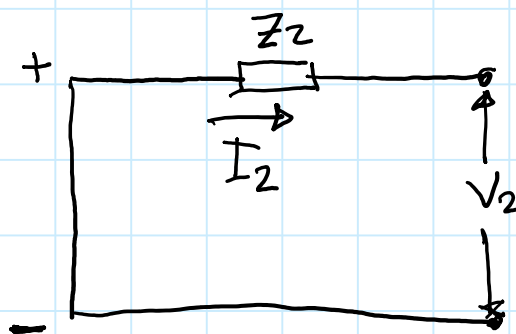




$$0 = I_2 Z_2 + V_2$$

ZERO SEQ NETWORK

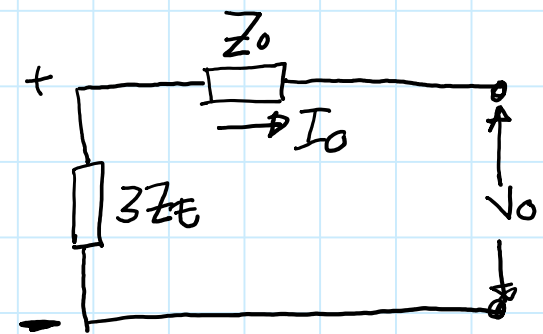

$$0 = I_0 Z_0 + 3Z_E I_0 + V_0$$



SINGLE LINE TO GROUND (PHASOR)

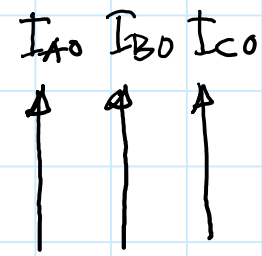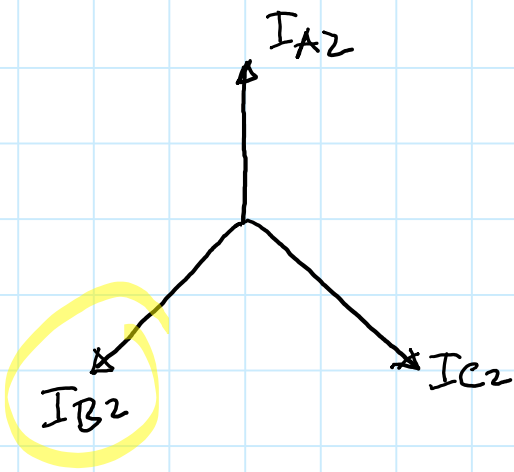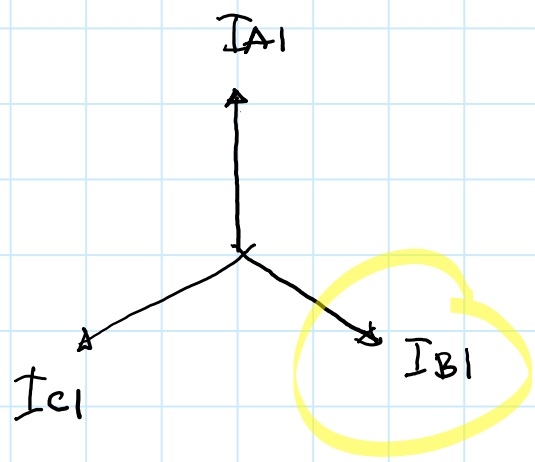


$$I_A = I_{A1} + I_{A2} + I_{A0}$$

$$I_B = I_{B1} + I_{B2} + I_{B0} = 0$$

$$I_C = I_{C1} + I_{C2} + I_{C0} = 0$$

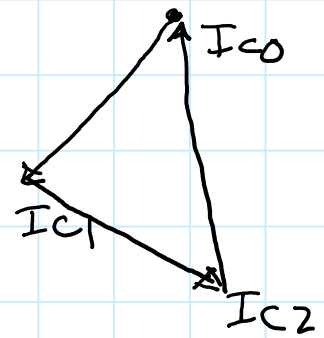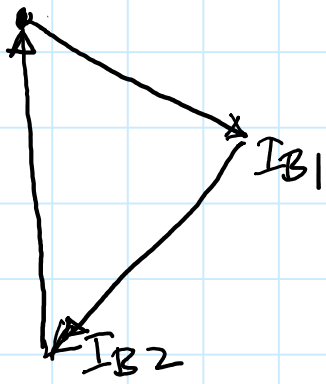

PHASE TO PHASE TO GROUND

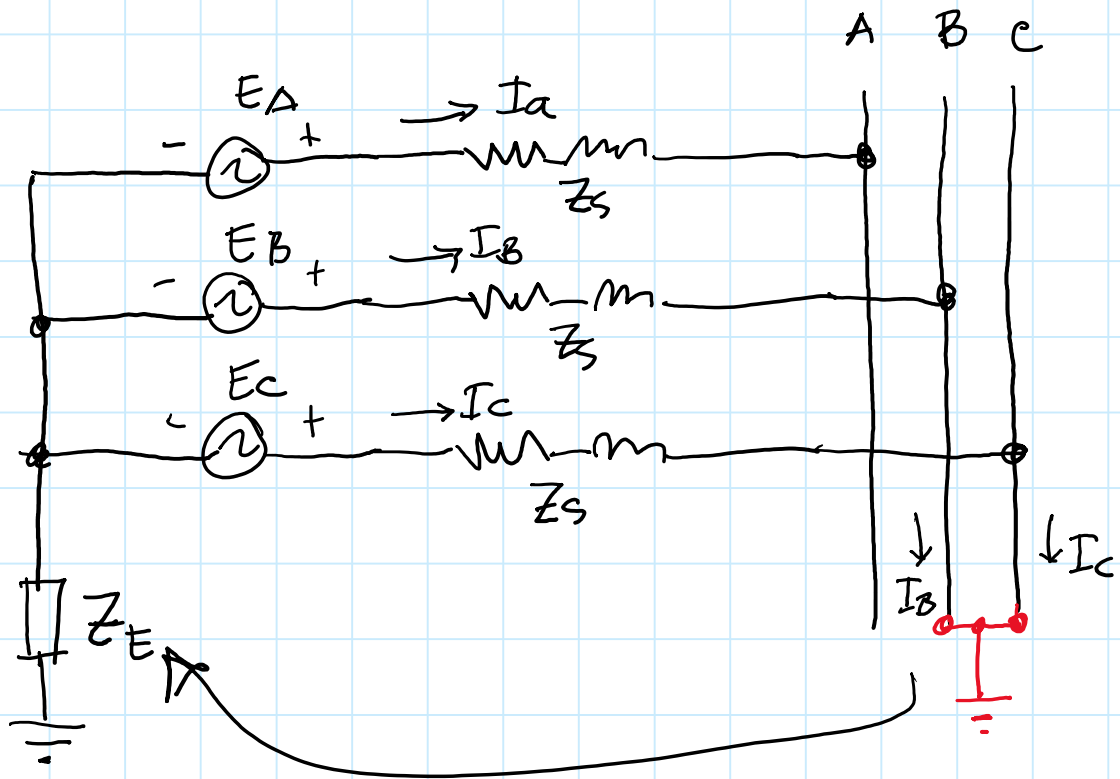

BOUNDARY CONDITIONS

$$I_A = 0 ; V_B = V_C = (I_B + I_C) Z_E$$

Taking phase A as reference (healthy phase):

$$I_{A0} = \frac{1}{3}(I_A + I_B + I_C) \quad \text{①}$$

$$V_B = V_C = 3I_{A0} Z_E$$

$$3I_0 = I_A + I_B + I_C \quad \text{②}$$

$$3I_1 = I_A + aI_B + a^2I_C \quad \text{③}$$

$$3I_2 = I_A + a^2I_B + aI_C \quad \text{④}$$

$$3V_0 = V_A + V_B + V_C \quad \text{⑤}$$

$$3V_1 = V_A + aV_B + a^2V_C \quad \text{⑥}$$

$$3V_2 = V_A + a^2V_B + aV_C \quad \text{⑦}$$

From eq ②

$$3V_0 = V_A + 2V_B$$

$$3V_1 = V_A + (a + a^2)V_B$$

$$3V_2 = V_A + (a + a^2)V_B$$

$$3V_0 = V_A + 2V_B = (V_{A0} + V_{A1} + V_{A2}) + 2(I_{A0} Z_E)$$

$$2V_0 = V_1 + V_2 + 2I_0 Z_E$$

$$\text{①} \quad V_1 = V_2 = \frac{1}{3}(V_A + aV_A + a^2V_B) = \frac{1}{3}(V_A + aV_C + a^2V_C)$$


$$\text{②} \quad 3V_0 = V_A + 2V_B = (V_0 + V_1 + V_2) + 2(3I_0 Z_E)$$

$$\text{①} + \text{②} \rightarrow 3V_0 = (V_0 + 2V_1) + 2(3I_0 Z_E)$$

$$2V_1 = 2V_0 - 2 \cdot 3I_0 Z_E$$

$$V_1 = V_0 - 3I_0 Z_E$$

$$V_1 = V_2 = V_0 - 3I_0 Z_E$$


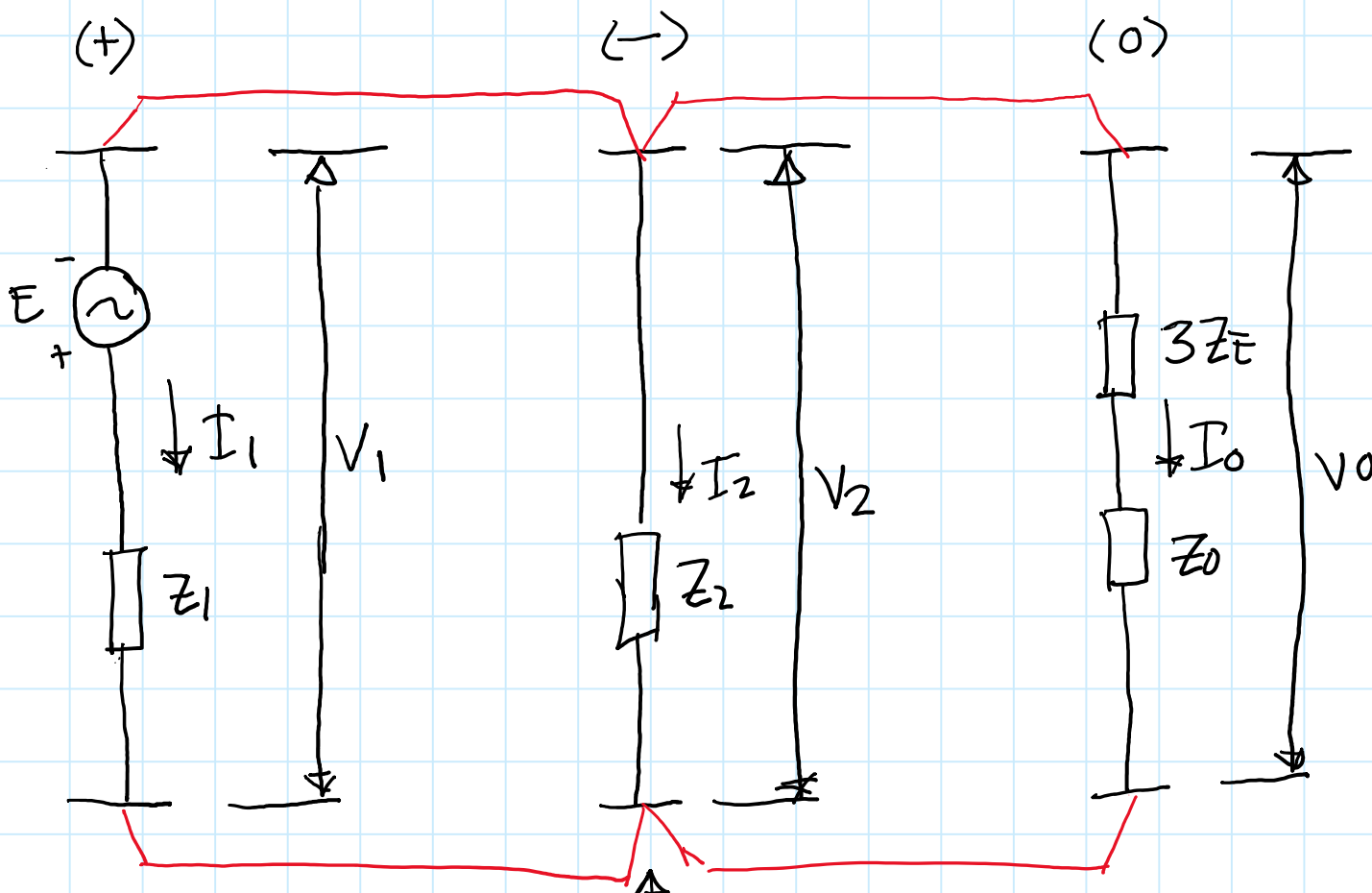


$$I_1 = \frac{E}{Z_1 + Z_2 \parallel Z_0}$$

$$I_1 + I_2 + I_0 = 0$$

$$I_1 = -(I_2 + I_0)$$

SEQUENCE NETWORK CONNECTIONS

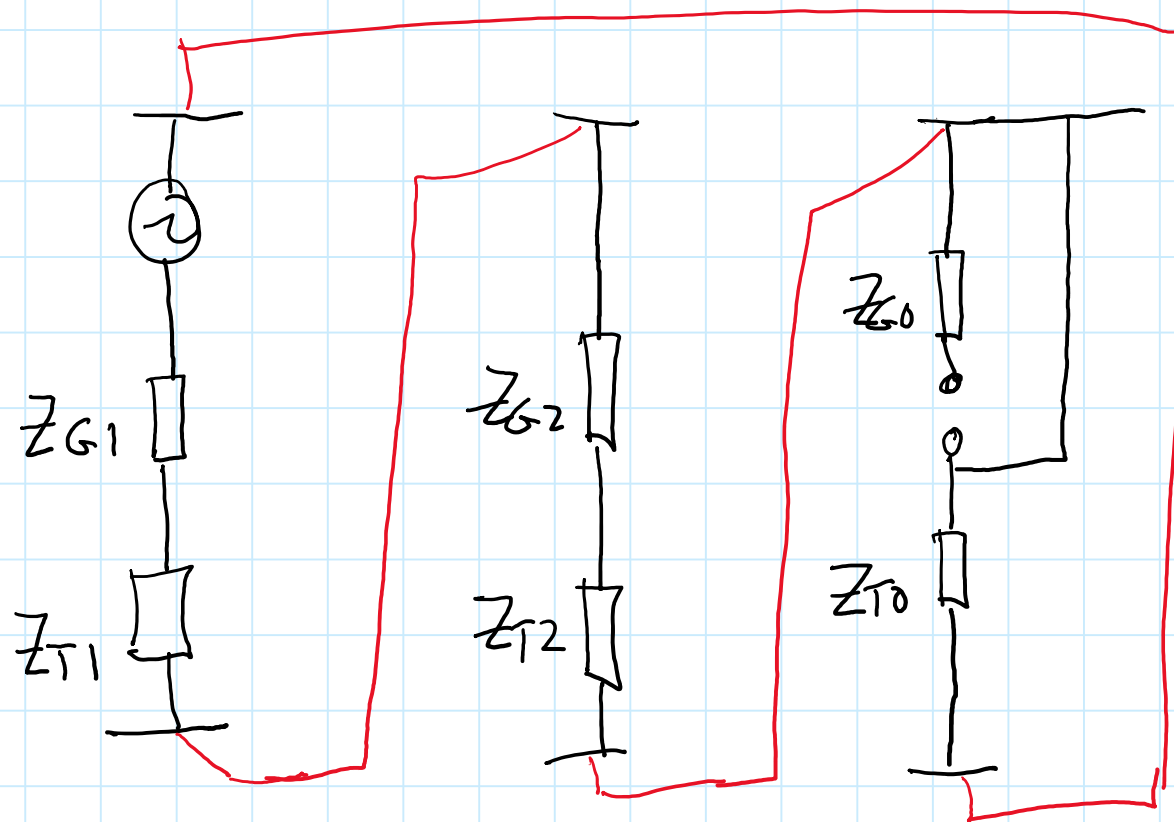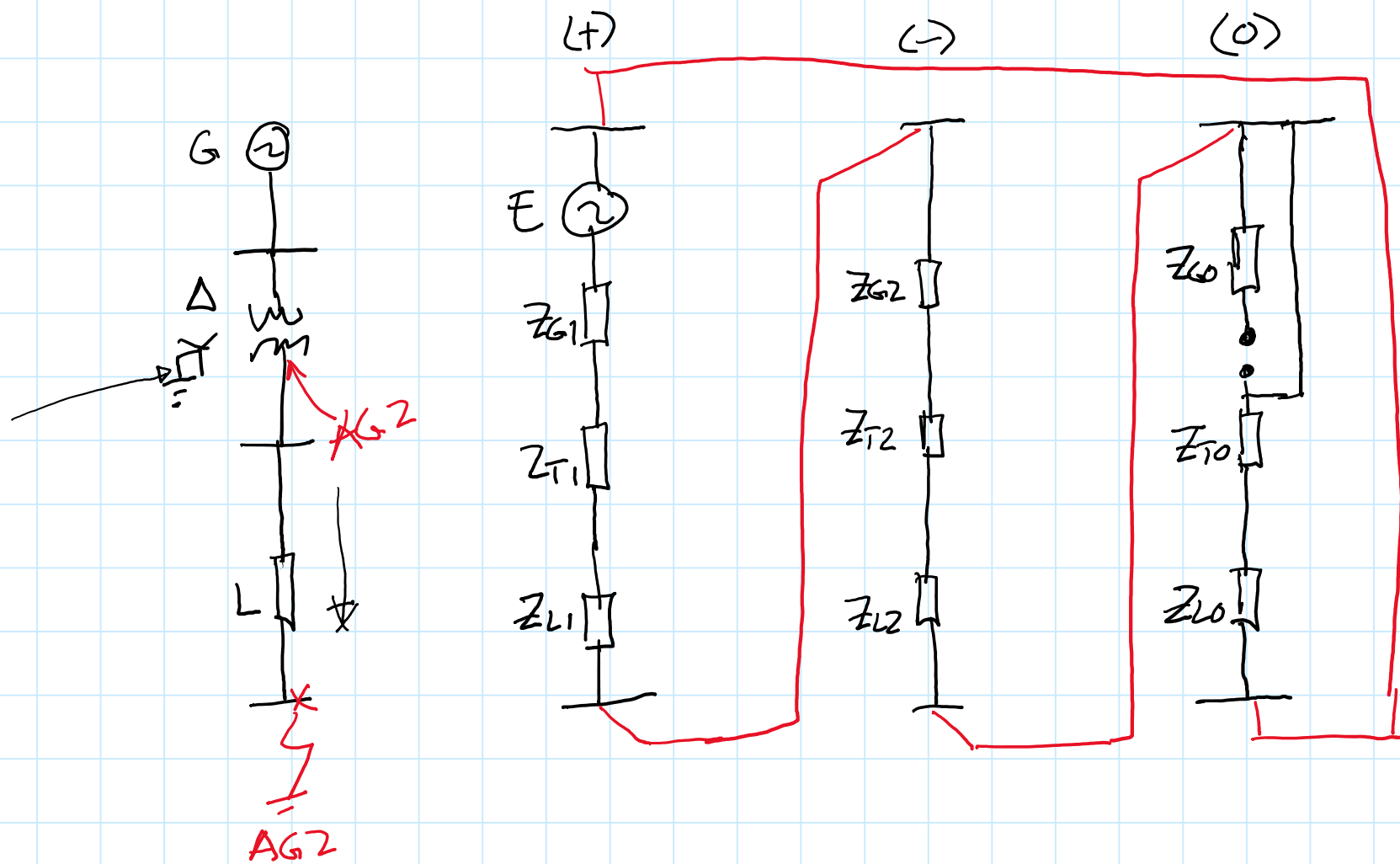

FOR 3 ϕ FAULT NEAR SEC SIDE OF XFMR

$$I_A = I_1 = \frac{E}{Z_{G1} + Z_{T1}}$$

$$Z_1 = Z_2 = Z_0$$

FOR SLG FAULT NEAR SEC SIDE OF XFMR

$$I_A = 3I_0 = \frac{3E}{Z_1 + Z_2 + Z_0 + 3Z_E} = \frac{3E}{Z_{G1} + Z_{T1} + Z_{G2} + Z_{T2} + Z_{T0}} = \frac{3E}{2Z_{G1} + 2Z_{T1} + Z_{T0}}$$




SOURCES OF FAULT CURRENTS

- ① UTILITY
- ② LOCAL GENERATORS
- ③ INDUCTION MOTORS
- ④ SYNCHRONOUS MOTORS

$\frac{1}{8}$ cycle

Interrupting
Asymmetrical RMS
Asymmetrical Peak

TWO SOURCE FEEDER SYSTEM

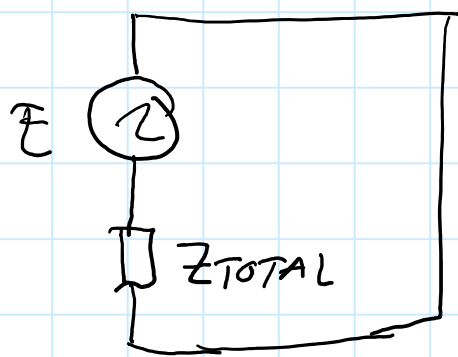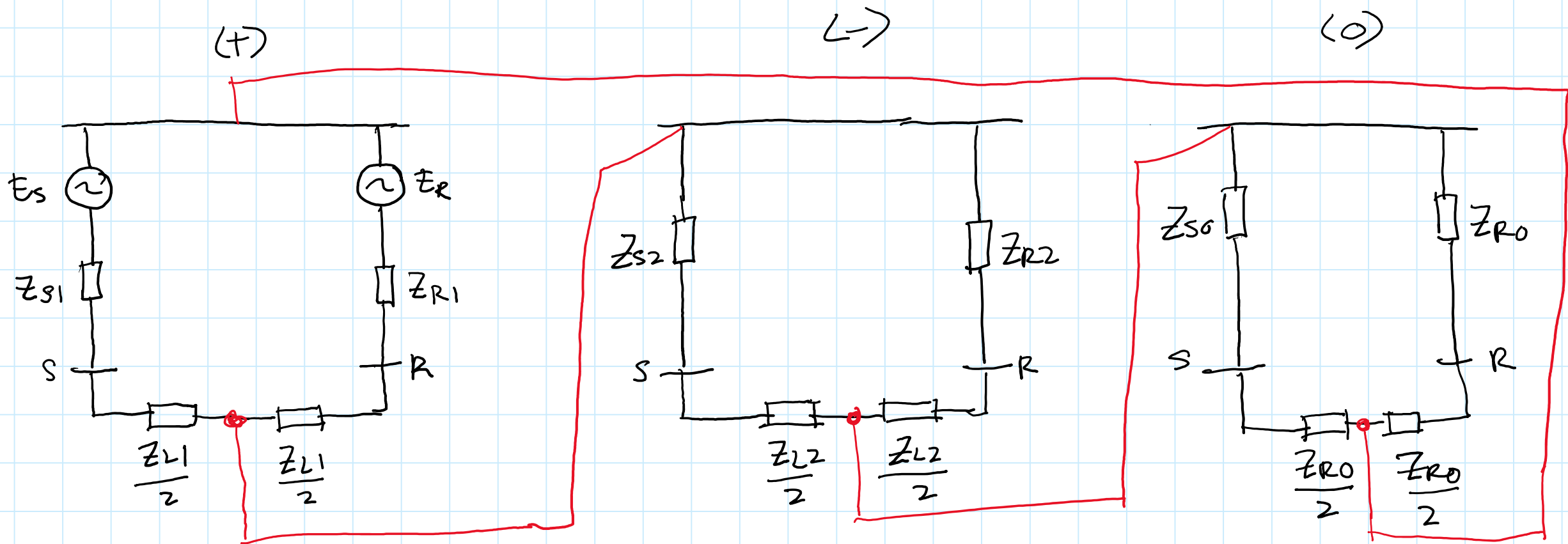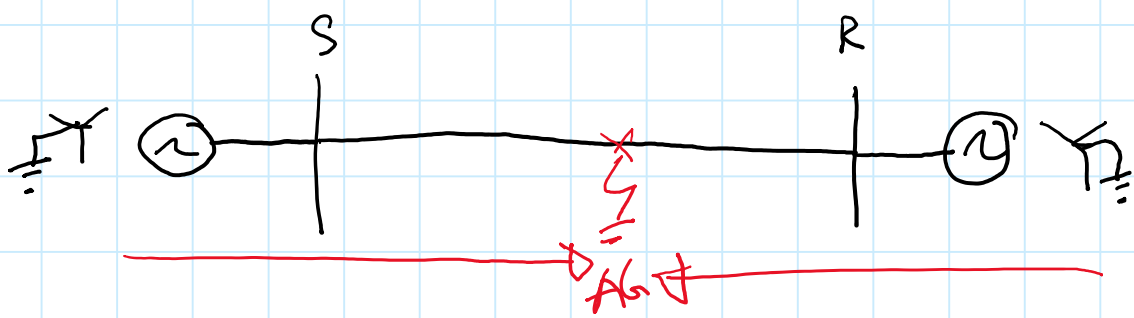

FOR MODERN RELAYS (a_0 and a_2 FACTORS)

$$a_0 = |I_0|/|I_1| \geq 0.10 \text{ declare SLG fault} \quad V_A = 0$$

$$a_2 = |I_2|/|I_1| \geq 0.10 \text{ declare LL fault} \quad V_B = V_C$$